

# Introduction to Verilog

Modules

Input/Output Ports

Basic Gates

Shorthand (Operators)

```
module <module-name>( portlist );
```

Declarations

...

Functional specification of module

...

```
endmodule
```

## Verilog Module Specifications

```
module light( x1, x2, f );  
    input x1, x2;  
    output f;  
    // Note: ~ means NOT  
    assign f = ( x1 & ~x2 ) | ( ~x1 & x2 );  
endmodule
```

Behavioral Verilog

# Verilog Code for Module light

```


module Light( X1, X2, F );
    input X1, X2;
    output F;

    wire X1_Bar, X2_Bar, Y1, Y2;

    // use built-in primitive gates (structural Verilog)
    // note: the order of these statements is not important
    or( F, Y1, Y2 );
    not( X1_Bar, X1 ),
        ( X2_Bar, X2 );
    and( Y1, X1, X2_Bar ),
        ( Y2, X1_Bar, X2 );
endmodule

```

Structural Verilog

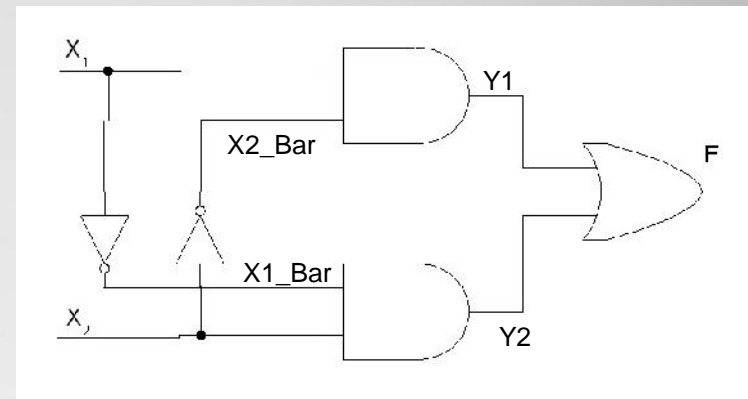

# Light Circuit Using Primitive Gates

Name	Usage	Name	Usage
and	and(f,a,b,...)	not	not(f,a)
nand	nand(f,a,b,...)	buf	buf(f,a)
or	or(f,a,b,...)	notif0	notif0(f,a,e) <sup>†</sup>
nor	nor(f,a,b,...)	notif1	notif1(f,a,e) <sup>†</sup>
xor	xor(f,a,b,...)	bufif0	bufif0(f,a,e) <sup>†</sup>
xnor	xnor(f,a,b,...)	bufif1	bufif1(f,a,e) <sup>†</sup>


<sup>†</sup> 'e' means enable; outputs not enabled are high-z

## Verilog Primitive Gates (Subset)


<code>~</code>	<code>~m</code>	invert each bit of m
<code>&amp;</code>	<code>m &amp; n</code>	AND each bit of m with each bit of n
<code> </code>	<code>m   n</code>	OR each bit of m with each bit of n
<code>^</code>	<code>m ^ n</code>	exclusive-OR each bit of m with n
<code>~^ or ^~</code>	<code>m ~^ n</code>	exclusive-NOR each bit of m with n
<code>&lt;&lt;</code>	<code>m &lt;&lt; n</code>	shift m left n-times and fill with zeros
<code>&gt;&gt;</code>	<code>m &gt;&gt; n</code>	shift m right n-times and fill with zeros

Note: m and n can be vectors

## Bitwise Verilog Operators

 

Quartus II RTL Viewer

 

Quartus Technology Map Viewer:  
What Actually Gets Loaded in the  
FPGA



- Comments:

```
// this is a comment
```

```
/* this is a comment - can span multiple  
lines */
```

- White space is ignored

Spaces

Tabs

new lines

## Comments and White Space in Verilog

- Verilog IS case sensitive: foo and Foo and fOO are all different.
- Any letter or digit may be used, as well as \_ and \$
- An identifier must not begin with a digit.
- An identifier must not be a Verilog keyword (refer to the Verilog HDL Quick Reference Guide section on Reserved Keywords – which are all lower case).
- Legal identifiers : f, x1, X1, x\_y
- Illegal identifiers : 1x, +y, 258j
- We will want our identifiers to start with capital letters! This is to distinguish them from keywords (at a glance).

## Identifier Names

Each signal in any of our circuits can take on one of four possible values:

0 = logic value 0 (false)

1 = logic value 1 (true)

z = tri-state (high impedance)

x = unknown value

## Signal Values

We'll talk about this in more depth later,  
but variables in Verilog can be scalars (one bit) or vectors.

Scalar:     

1
---

 or 

0
---

 or 

z
---

 or 

x
---

     Example: `wire S1;`

Vector:     

1	1	0	1
---	---	---	---

     (four-bit vector)     Example: `wire[3:0] V1;`

## Vectors

- A **vector** data type defines a collection of bits.
- The **range specification** defines the numbering and order of the bits [msb:lsb].
- [3:0] A → Little endian convention
- [0:3] A → Big endian convention
- [1:4] A → legal, but unconventional
- Use [3:0] A unless there's a good reason to do otherwise.
- Use A[2] (for example) to select individual bits.
- Use A[2:1] to select bits 2 and 1.

## Vectors

<code>~</code>	<code>~m</code>	invert each bit of m
<code>&amp;</code>	<code>m &amp; n</code>	AND each bit of m with each bit of n
<code> </code>	<code>m   n</code>	OR each bit of m with each bit of n
<code>^</code>	<code>m ^ n</code>	exclusive-OR each bit of m with n
<code>~^ or ^~</code>	<code>m ~^ n</code>	exclusive-NOR each bit of m with n
<code>&lt;&lt;</code>	<code>m &lt;&lt; n</code>	shift m left n-times and fill with zeros
<code>&gt;&gt;</code>	<code>m &gt;&gt; n</code>	shift m right n-times and fill with zeros

Note: m and n can be vectors

## Bitwise Verilog Operators

```
// TCES 330, Spring 2011
// R. Gutmann
// This module illustrates a simple vector operation

module SimpleVector( SW, LEDR );
    input [17:0] SW;      // vector input
    output [17:0] LEDR;   // vector output

    wire [17:0] Temp;     // temporary variable

    assign Temp = ~SW;

    assign LEDR = Temp;

    // Note: have been assign LEDR = ~SW;

endmodule
```

## Simple Vector Example



RTL View of SimpleVector



<b>&amp;</b>	<code>&amp;m</code>	AND all bits in m together (1-bit result)
<b>~&amp;</b>	<code>~ &amp;m</code>	NAND all bits in m together (1-bit result)
<b> </b>	<code>  m</code>	OR all bits in m together (1-bit result)
<b>~ </b>	<code>~   m</code>	NOR all bits in m together (1-bit result)
<b>^</b>	<code>^m</code>	exclusive-OR all bits in m (1-bit result)
<b>~^ or ^~</b>	<code>~ ^m</code>	exclusive-NOR all bits in m (1-bit result)

Note: m is a vector

## Verilog Reduction Operators


```
// TCES 330, Spring 2011
// R. Gutmann
// This module illustrates a simple vector reduction operation
//
module SimpleVector( SW, LEDR );
    input [17:0] SW;    // vector input

    output [0:0] LEDR; // scalar output

    assign LEDR[0] = ^SW;

endmodule
```

## Vector Reduction Example

 

RTL View of VectorReduction

<b>!</b>	<code>!m</code>	is m not true? (1-bit True/False result)
<b>&amp;&amp;</b>	<code>m &amp;&amp; n</code>	are both m and n true? (1-bit True/False result)
<b>  </b>	<code>m    n</code>	are either m or n true? (1-bit True/False result)

## Verilog Logical Operators

<b>Equality and Relational Operators (return X if an operand has X or Z)</b>		
<b>==</b>	<code>m == n</code>	is m equal to n? (1-bit True/False result)
<b>!=</b>	<code>m != n</code>	is m not equal to n? (1-bit True/False result)
<b>&lt;</b>	<code>m &lt; n</code>	is m less than n? (1-bit True/False result)
<b>&gt;</b>	<code>m &gt; n</code>	is m greater than n? (1-bit True/False result)
<b>&lt;=</b>	<code>m &lt;= n</code>	is m less than or equal to n? (1-bit True/False result)
<b>&gt;=</b>	<code>m &gt;= n</code>	is m greater than or equal to n? (1-bit True/False result)
<b>Identity Operators (compare logic values 0, 1, X, and Z)</b>		
<b>===</b>	<code>m === n</code>	is m identical to n? (1-bit True/False results)
<b>!==</b>	<code>m !== n</code>	is m not identical to n? (1-bit True/False result)

## Verilog Relational Operators

<code>? :</code>	<code>sel ?m:n</code>	conditional operator; if sel is true, return m: else return n
<code>{ }</code>	<code>{m,n}</code>	concatenate m to n, creating a larger vector
<code>{ { }</code>	<code>{n{ } }</code>	replicate inner concatenation n-times
<code>-&gt;</code>	<code>-&gt; m</code>	trigger an event on an event data type

## Miscellaneous Verilog Operators

```
// TCES 330, Spring 2011
// R. Gutmann
// This module illustrates the replication operator
//
module MiscOperator( SW, LEDR );
    input [0:0] SW;      // scalar input

    output [17:0] LEDR; // vector output

    assign LEDR = {18{SW[0]}}; // replicate SW[0] 18 times
endmodule
```

## Miscellaneous Operators Example



# RTL View of MiscOperators



Arithmetic Operators		
+	$m + n$	add n to m
-	$m - n$	subtract n from m
-	$-m$	negate m (2's complement)
*	$m * n$	multiply m by n
/	$m / n$	divide m by n
%	$m \% n$	modulus of m / n
**	$m ** n$	m to the power n (new in Verilog-2001)
<<<	$m <<< n$	shift m left n-times, filling with 0 (new in Verilog-2001)
>>>	$m >>> n$	shift m right n-times; fill with value of sign bit if expression is signed, otherwise fill with 0 (Verilog-2001)


## Verilog Arithmetic Operators

!	~	+	- (unary)	highest precedence
{ }	{ { } }			
( )				
**				
*	/	%		
+	-		(binary)	
<<	>>	<<<	>>>	
<	<=	>	>=	
==	!=	===	!==	
&	~&			
^	~^			
	~			
&&				
?:				lowest precedence

# Operator Precedence

Pretty much as you would expect, but use parentheses to make it clear!

## 2-to-1 Mux

 


X0 and X1 are the inputs

S is a 'select' bit


F is the output

$F = X0$  if  $S=0$ ;  $F = X1$  if  $S=1$

# 2-to-1 Multiplexer (Mux)

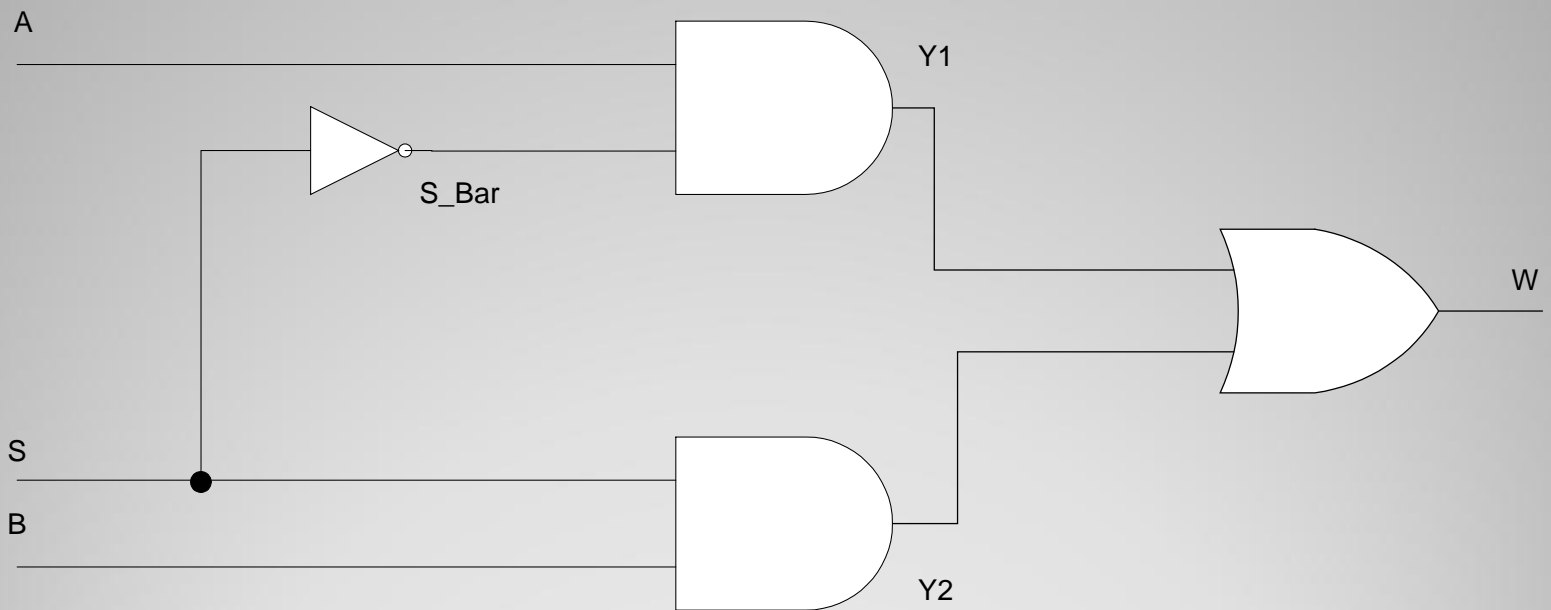


2-to-1 Multiplexer

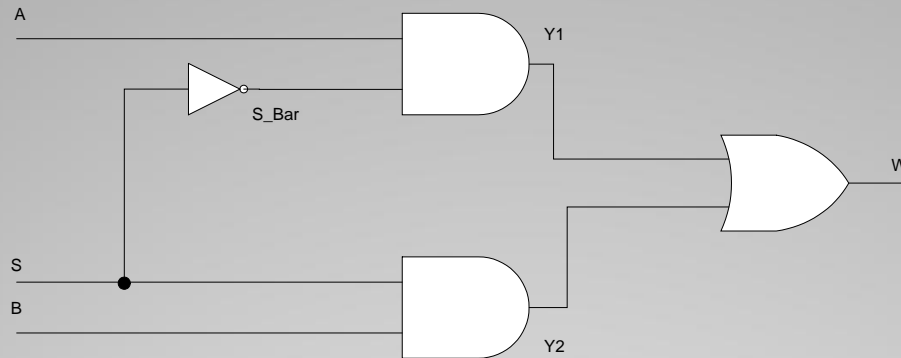


```
module Mux2to1A( A, B, S, W );  
    input A, B, S;  
    output W;  
  
    wire S_Bar, Y1, Y2;  
  
    // use built-in primitive gates  
    not U1( S_Bar, S );  
    and U2( Y1, A, S_Bar );  
    and U3( Y2, B, S );  
    or U4( W, Y1, Y2 );  
endmodule
```

Mux2to1A.v

 

RTL View of Mux2to1

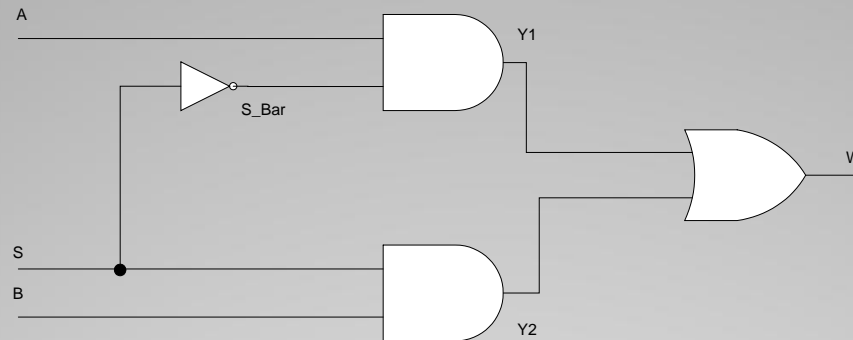


```
module Mux2to1B( A, B, S, W );  
    input A, B, S;  
    output W;  
    // using assign and boolean operators  
    assign W = ( A & ~S ) | ( B & S );  
endmodule
```

Mux2to1B.v

```
module Mux2to1C( A, B, S, W );  
    input A, B, S;  
    output W;  
  
    // using assign and conditional operator  
    assign W = S ? B : A;  
endmodule
```

Mux2to1C.v




 

RTL View of Mux2to1C

```
module Mux2to1D( A, B, S, W )  
  input A, B, S;  
  output reg W;  
  // using a procedure  
  always @( A, B, S ) begin  
    if ( S ) W = B;  
    else W = A;  
  end  
endmodule
```

Mux2to1D.v

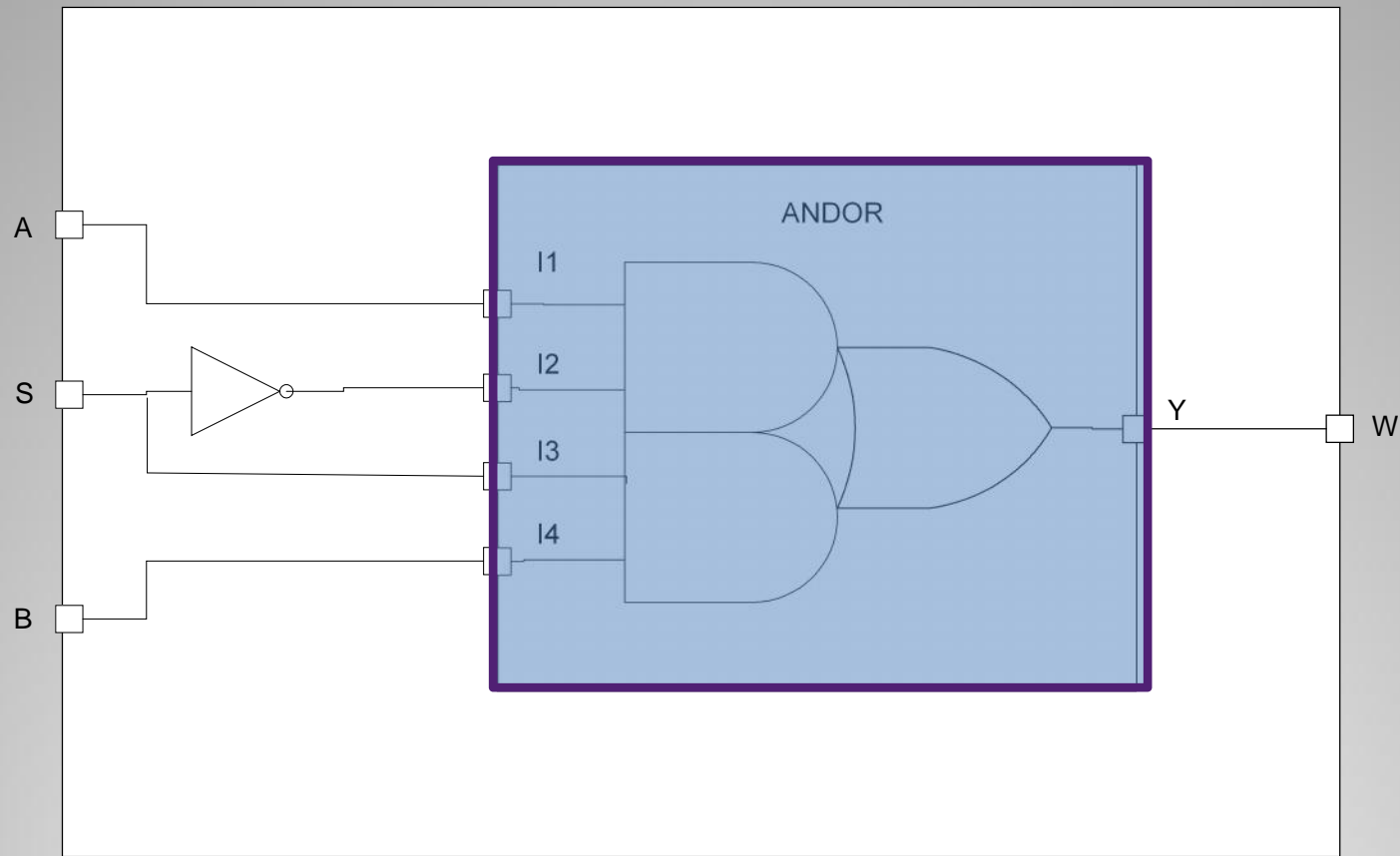

2-to-1 Mux Using ANDOR Module

```
module ANDOR( input I1, I2, I3, I4, output Y );  
    assign Y = ( I1 & I2 ) | ( I3 & I4 );  
endmodule
```


Note the “input” and “output” designation in the module’s port list.  
This is an optional way of specifying the inputs and outputs.

ANDOR.v

```
module Mux2to1E( A, B, S, W );  
    input A, B, S;  
    output W;  
  
    wire S_Bar = ~S;  
  
    // make an instance of ANDOR:  
    ANDOR U1( A, S_Bar, S, B, W );  
endmodule
```

Mux2to1E.v
 
## Vector inputs and outputs: 8-Wide 2-to-1 Mux



X0 and X1 are the inputs

S is a 'select' bit

F is the output

$F = X0$  if  $S == 0$ ;  $F = X1$  if  $S == 1$

# 2-to-1 Multiplexer (Mux)

$A = X3(X1 + X2')$   
 $B = X1(X2' + X3')$   
 $C = X2(X1 + X3')$

$F = AB + AC + BC$

after some algebra...  
 $F = X1(X3 + X2)$


```
// compute A, B, C
assign A = X3 & ( X1 | ~X2 );
assign B = X1 & ( ~X2 | ~X3 );
assign C = X2 & ( X1 | ~X3 );

// compute F
assign F = A&B | A&C | B&C;
```

[Quartus II Project](#)

## Example 2.10

(B&V Page 67)

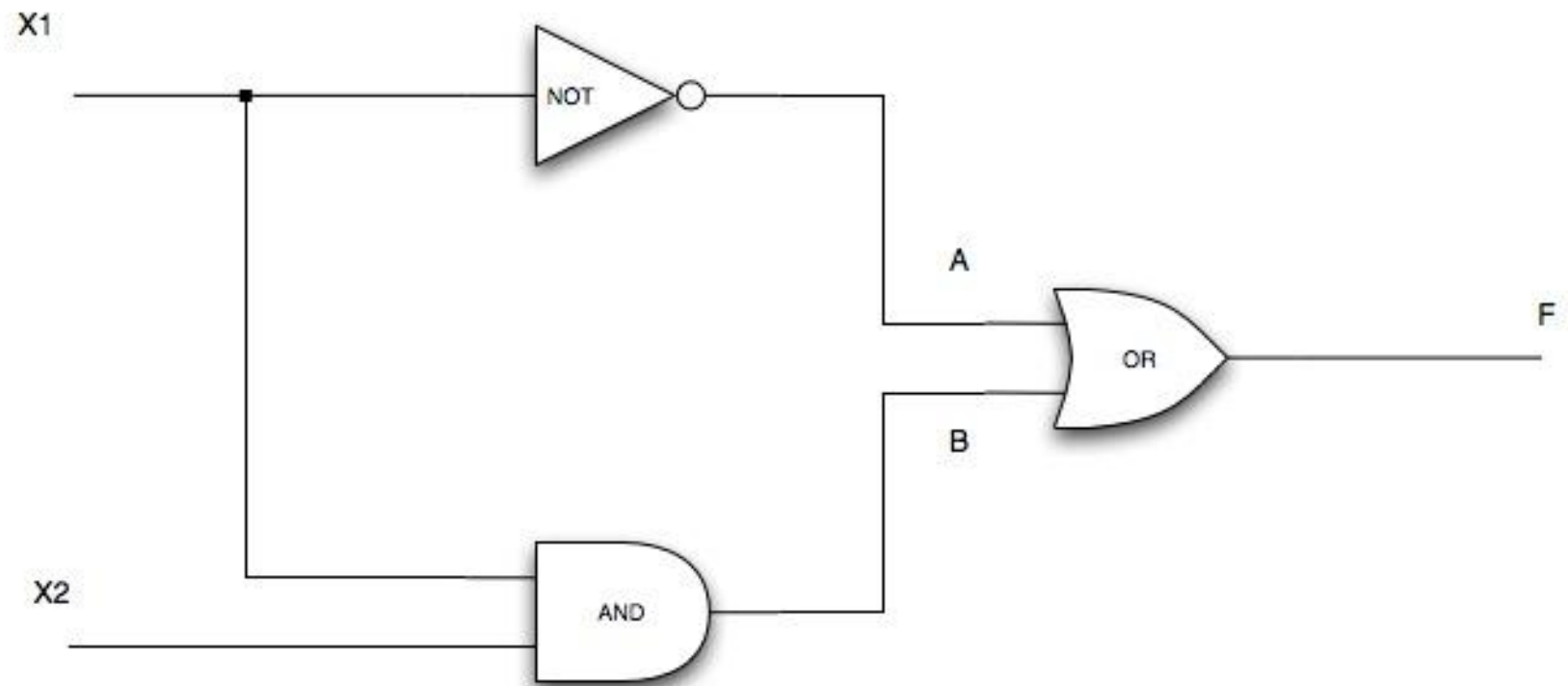


B&V Figure 2.1.0

B&V Figure 2.10a



- The Lab0 tutorial tells you how to import pin assignments. Look on page 22 at the sentence that begins “You can import a pin assignment...”
- The file you want to import is DE2\_pin\_assignments.csv. This file is up on the Moodle site. And you can copy it to whatever folder you are using for Lab 1, Part 1.
- The Lab 1 Part 1 write-up also talks about using DE2\_pin\_assignments.csv
- After you import this file and recompile, you will get lots of warnings about pins you’ve assigned but not used. We will deal with this issue later.

## Pin Assignments

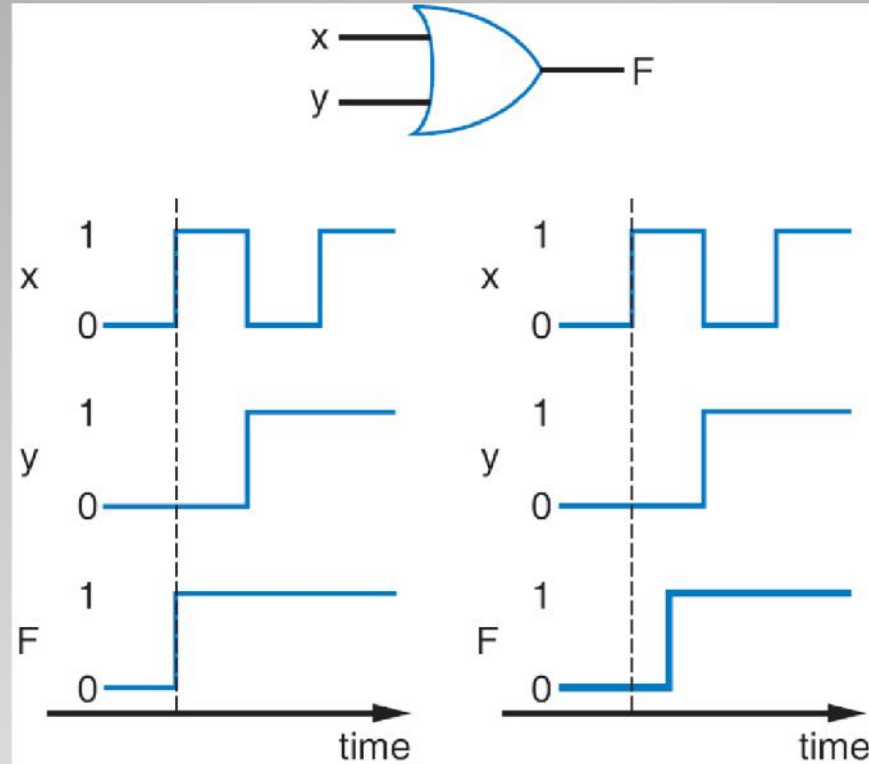

- Real gates have some delay  
Outputs don't change immediately after inputs change

## Additional Considerations

Non-Ideal Gate Behavior -- Delay