

TCES 330

Lecture 14

When you use the Compiler to perform a full compilation, the Compiler uses a series of modules to process the design and, ultimately, to create one or more programming files.

- [Analysis & Synthesis](#), which first checks the design files and the overall design for errors, and builds a single design database that integrates all the design files in a design hierarchy. Analysis & Synthesis performs logic synthesis to minimize the logic of the design, and performs technology mapping to implement the design logic using device resources such as logic elements. Analysis & Synthesis provides comprehensive Verilog HDL and VHDL language support..
- The [Fitter](#), which fits (that is, places and routes) the logic of a design into a device. You must perform analysis and synthesis on a design before using the Fitter. When you use the Fitter on a design, the Fitter runs an Auto Fit compilation by default. In Auto Fit mode, the Fitter attempts to meet your timing constraints and not to beat them; it automatically decreases compilation time by turning off some optimization steps if they are not required for the design to meet the timing constraints. You can also decrease compilation time by directing the Fitter to reduce Fitter effort after meeting a design's timing requirements, or to make only one fitting attempt.

What Quartus 'Compile' Mean?

- The [Assembler](#), which converts the Fitter's device, logic cell, and pin assignments into a programming image for the device. The Assembler is the Compiler module that completes project processing by converting the Fitter's device, logic cell, and pin assignments into a device programming image, in the form of one or more Programmer Object Files (.pof), SRAM Object Files (.sof), Hexadecimal (Intel-Format) Output Files (.hexout), Tabular Text Files (.tff), and Raw Binary Files (.rbf), from a successful fit.
- The [Design Assistant](#), which checks the reliability of a design based on a set of design rules. You can use the Design Assistant after either performing Analysis & Synthesis or using the Fitter on a design.
- The TimeQuest [Timing Analyzer](#), which analyzes, debugs, and validates the timing performance of all logic in a design. You must complete Analysis & Synthesis and Fitting on a design before performing a full timing analysis. However, you can [run an early timing estimate](#) to obtain preliminary timing data without completing fitting.

Quartus 'Compile', cont.

State Machines, Continued

SAD Processor




Mythbusters Frame 1



Mythbusters Frame 2

- Compare small patches, one frame to the next.
- If changes are minor, just send the difference between the patches.
- If changes are not minor, send the whole patch.
- 'Patches' are 16 x 16 pixel blocks (256 pixels).
- In our simplified example each pixel is one byte (8 bits).
- We'll take the difference between each pair of pixels
- We'll take the absolute value of this difference.
- We'll sum up all these values for the patch (SAD).
- If this value is less than some threshold, we'll just send the difference, otherwise the whole patch.

One Aspect of Video Compression

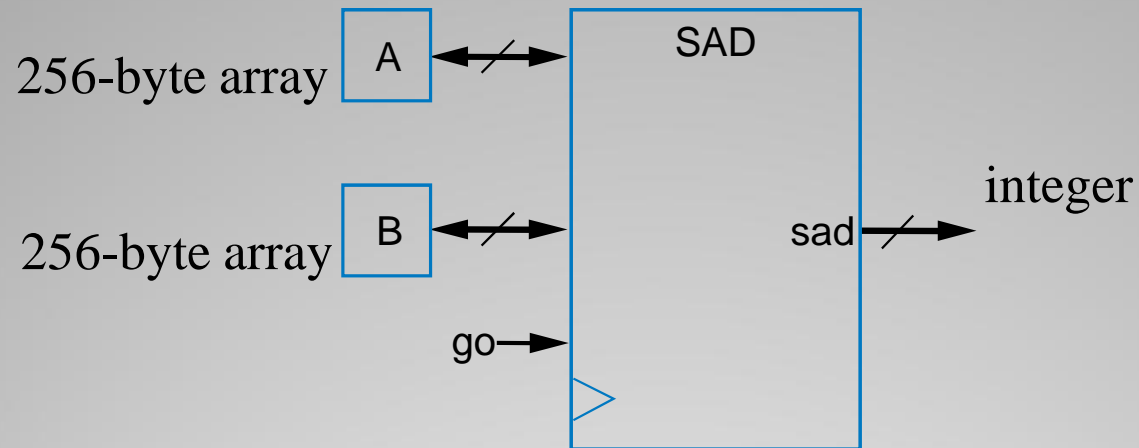


- Want fast sum-of-absolute-differences (SAD) component
 - When $go=1$, sums the absolute value of the differences of element pairs in arrays A and B, outputs that sum

- $$sad = \sum_{i=0}^{255} |A_i - B_i|$$



SAD Circuit

 


Inputs: A, B (256 byte memory); go (bit)

Outputs: sad (32 bits)

Local registers: sum, sad_reg (32 bits); i (9 bits)

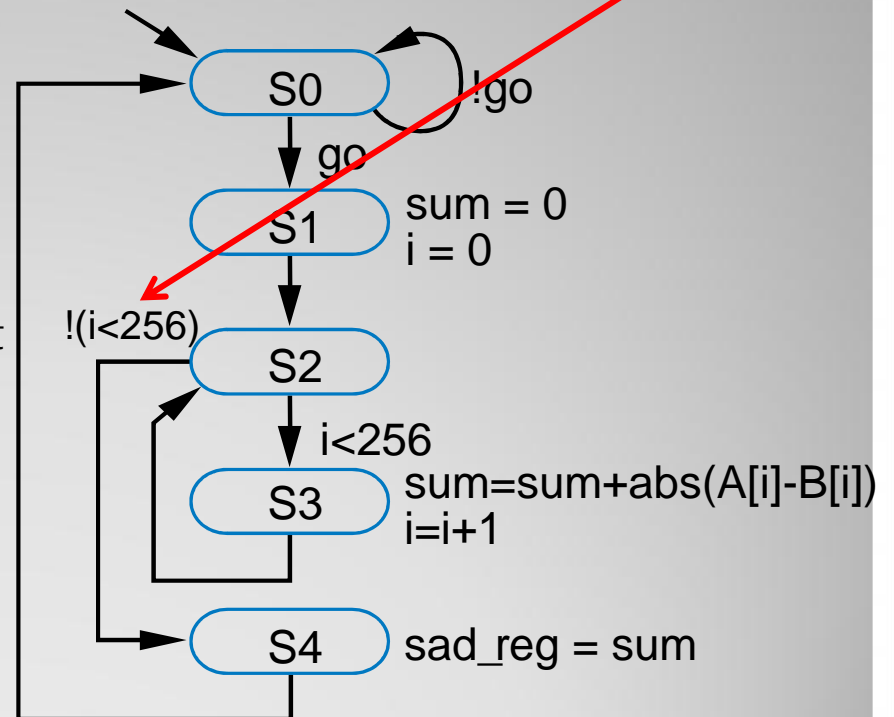- S0: wait for go
- S1: initialize sum and index
- S2: check if done ($i \geq 256$)
- S3: add difference to sum, increment index
- S4: done, write to output sad_reg



SAD State Machine

From F. Vahid's *Digital Design*

- Verilog Task

A task is declared by the keyword task and it comprises a block of statements that ends with the keyword endtask. The task must be included in the module that calls it. It may have input and output ports (these are not the ports of the module that contains the task). The task ports are used only to pass values between the module and the task.

- Verilog Function

A function is declared by the keyword function and it comprises a block of statements that ends with the keyword endfunction. The function must have at least one input and it returns a single value that is placed where the function is invoked.

Verilog Tasks and Functions

```

module mux16to1 (W, S16, f);
    input [15:0] W;    // 16 inputs
    input [3:0] S16;  // 4 bits of select
    output reg f;      // 1 bit of output

    always @( W, S16 )
        case ( S16[3:2] )
            0: mux4to1( W[3:0],    S16[1:0], f );
            1: mux4to1( W[7:4],    S16[1:0], f );
            2: mux4to1( W[11:8],   S16[1:0], f );
            3: mux4to1( W[15:12],  S16[1:0], f );
        endcase
    end // always
// Task that specifies a 4-to-1 multiplexer
task mux4to1;
    input [0:3] X;
    input [1:0] S4;
    output reg g;

    case (S4)
        0: g = X[0];
        1: g = X[1];
        2: g = X[2];
        3: g = X[3];
    endcase
endtask
endmodule

```

Use of a Task in Verilog

- Intuitive example: Washing dishes with a friend, you wash, friend dries

You wash plate 1


Then friend dries plate 1, while you wash plate 2

Then friend dries plate 2, while you wash plate 3; and so on

You don't sit and watch friend dry; you start on the next plate

- **Pipelining:** Break task into stages, each stage outputs data for next stage, all stages operate concurrently (if they have data)


Pipelining

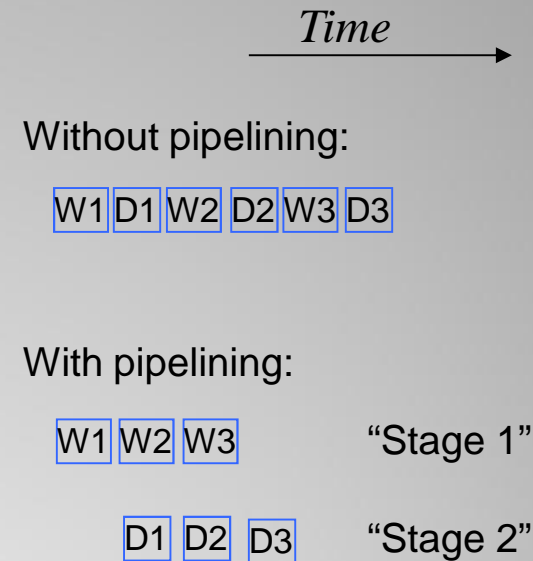

More Datapath

- What do we count? Clock pulses, **always!**
- Not necessarily every clock pulse.
- If we want to count the output pulses from some other circuit, we use those pulses to **enable** our clock pulse counter.
- We use counters to add delays or timers to our circuits
 - Not for-loops
 - Not while-loops
 - Not wait-statements
- All modern μ Processor controllers have built-in timers (counters).


Counters/Timers

 

Arithmetic Logic Unit (ALU)

6.2 Architectural Overview

Figure 6-1: Block Diagram of the AVR Architecture

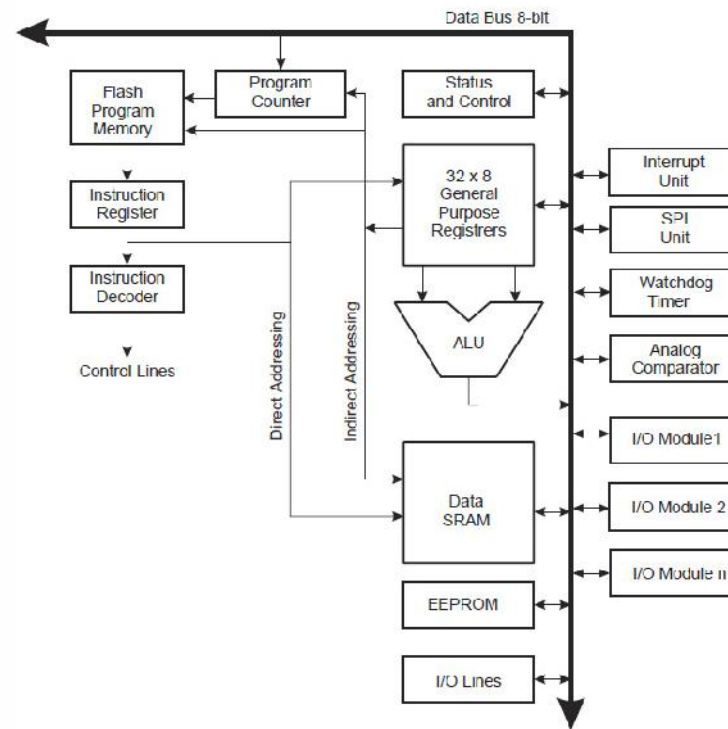

Atmel 168 Microprocessor

TABLE 4.2 Desired calculator operations

Inputs			Operation	Sample output if A=00001111, B=00000101
x	y	z		
0	0	0	$S = A + B$	S=00010100
0	0	1	$S = A - B$	S=00001010
0	1	0	$S = A + 1$	S=00010000
0	1	1	$S = A$	S=00001111
1	0	0	$S = A \text{ AND } B$ (bitwise AND)	S=00000101
1	0	1	$S = A \text{ OR } B$ (bitwise OR)	S=00001111
1	1	0	$S = A \text{ XOR } B$ (bitwise XOR)	S=00001010
1	1	1	$S = \text{NOT } A$ (bitwise complement)	S=11110000

Example Arithmetic Logic Unit

```

module ALU( Sel, A, B, S );
  input [2:0] Sel; // function select
  input [7:0] A, B; // input data
  output reg [7:0] S; // ALU output (result)

  always @ * begin
    S = 0; // default value
    case ( Sel )
      3'h0: begin
        S = A + B; // ADD
      end
      3'h1: begin
        S = A - B; // SUBTRACT
      end
      3'h2: begin
        S = A + 1'b1; // INCREMENT
      end
      3'h3: begin
        S = A; // FALL-THROUGH
      end
    endcase
  end
endmodule

```

```

      3'h4: begin
        S = A & B; // bitwise AND
      end
      3'h5: begin
        S = A | B; // bitwise OR
      end
      3'h6: begin
        S = A ^ B; // bitwise XOR
      end
      3'h7: begin
        S = ~ A; // bitwise complement
      end
    endcase
  end // always
endmodule


```

Simple ALU in Verilog

- We would write more general Verilog (N bits)
- We would output the usual flags
 - Zero
 - Overflow
 - Negative
 - Etc.
- Additional functions
 - Compare (signed and unsigned)
 - Shifts and Rotates left and right
 - Increment/decrement
 - ...

ALU Improvements


Register Files

 

- Recall: Four simultaneous values from car's computer
- To reduce wires: Computer writes only 1 value at a time, loads into one of four registers


Was: $8+8+8+8 = 32$ wires

Now: $8 + 2 + 1 = 11$ wires

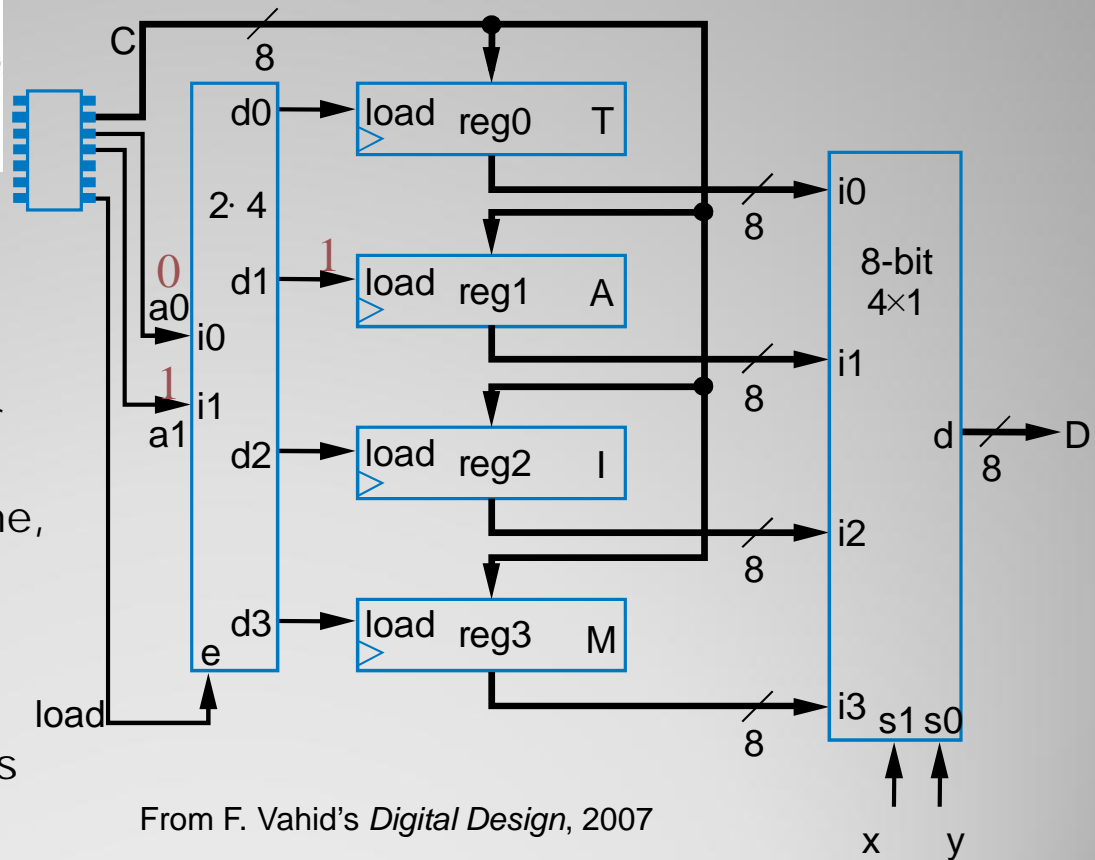

From F. Vahid's *Digital Design*, 2007


Recall: Above-Mirror Display

 


What Quartus Built

What if we had **16 32-bit registers** to deal with?

 - Lots of input fan-out
- Mux would have to have lots of input lines
- Large Muxes are slow




Wide Register Bank

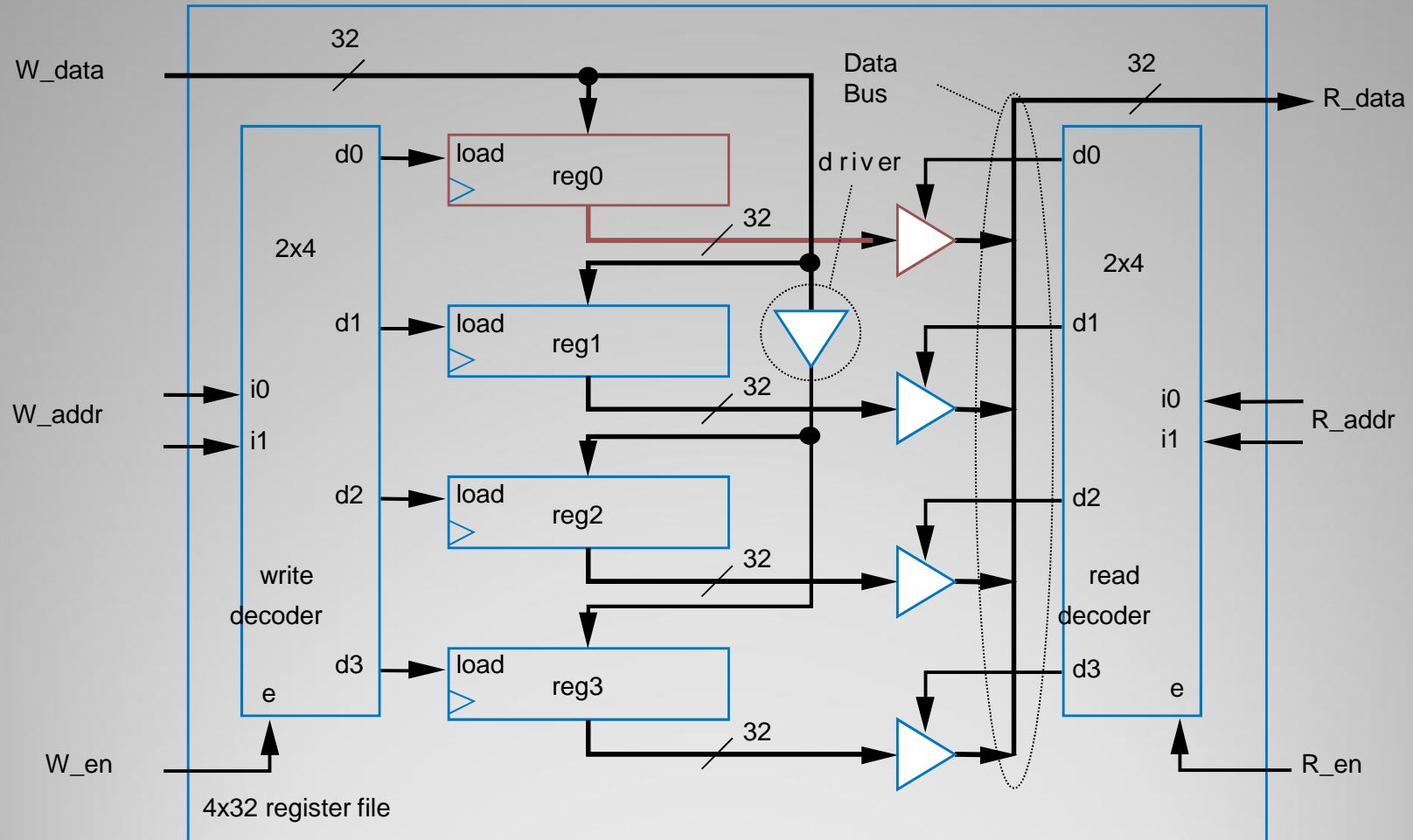

From F. Vahid's Digital Design, 2007

Register with Output Enable

 

Register with OE Detail

```

module RegisterOE4( Clk, Rst, Ld, I, Oe, Qz );
    input Clk;
    input Rst;
    input Ld;          // load signal
    input Oe;          // output enable (this is new)
    input [3:0] I;     // data to load


    output [3:0] Qz; // switched output
    reg [3:0] Q;      // standard register variable

    // Register Procedure
    always @(posedge Clk) begin
        if (Rst == 1)      // reset
            Q <= 0;
        else if (Ld == 1) // load
            Q <= I;
        end

    // Output
    assign Qz = Oe ? Q : 4'bzzzz;
endmodule

```

4-Bit Register with Output Enable

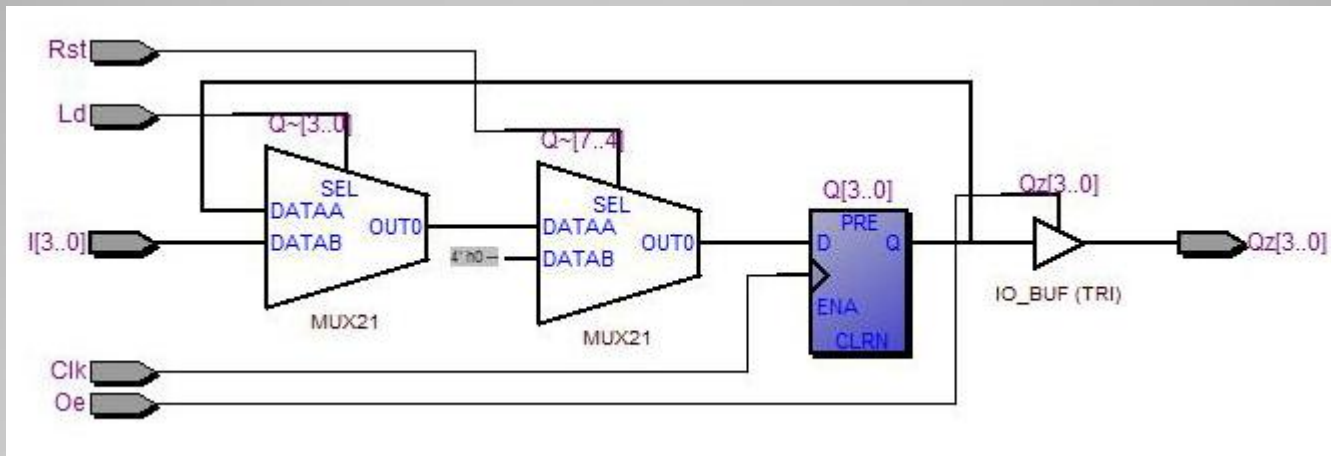

What Quartus Built

How do we generalize the
RegisterOE module to an N-
Bit Register?

```

module RegisterOE( I, Ld, Oe, Clk, Rst, Q );
    input [31:0] I;    // data to load
    input Ld;          // load signal
    input Oe;          // output enable (this is new)
    input Clk, Rst;
    output [31:0] Q;   // our output
    reg [31:0] R;      // the basic register
    // Register Procedure
    always @(posedge Clk) begin
        if (Rst == 1)
            R <= 0;
        else if (Ld == 1)
            R <= I;
    end

    // Output
    assign Q = Oe ? R : 32'hZZZZZZZZ;

endmodule

```

These sizes must agree
(and N'bZ is not valid)

Register with Output Enable

```

module RegisterOEN( Clk, Rst, Ld, I, Oe, Qz );
    parameter N = 4;

    input Clk;
    input Rst;
    input Ld;           // load signal
    input Oe;           // output enable (this is new)
    input [N-1:0] I;    // data to load

    output [N-1:0] Qz;  // switched output
    reg [N-1:0] Q;      // the basic register


    // Register Procedure
    always @(posedge Clk) begin
        if (Rst == 1)
            Q <= 0;
        else if (Ld == 1)
            Q <= I;
    end

    // Output
    assign Qz = Oe ? Q : {N{1'bZ}};

endmodule

```


RegisterOEN

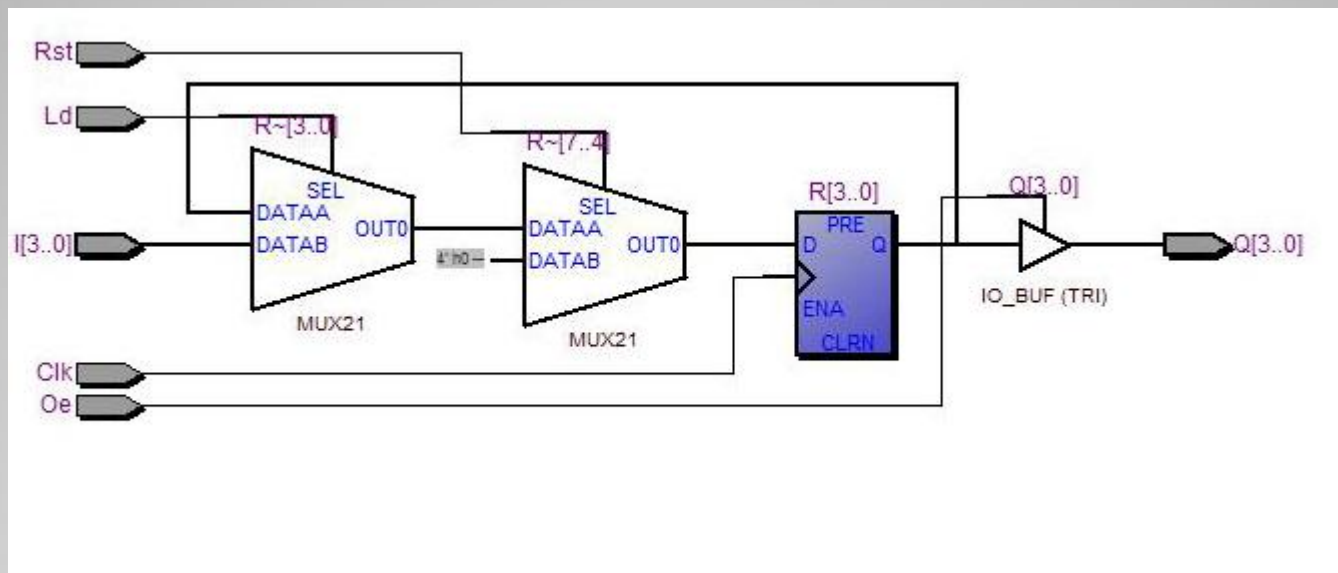


RegisterOEN with $N = 4$

- For our register file we'll need:
 - Decoder for write
 - Decoder for read
 - Registers with output enable
 - Drivers (Quartus will take care of these for us)

Building the Register File

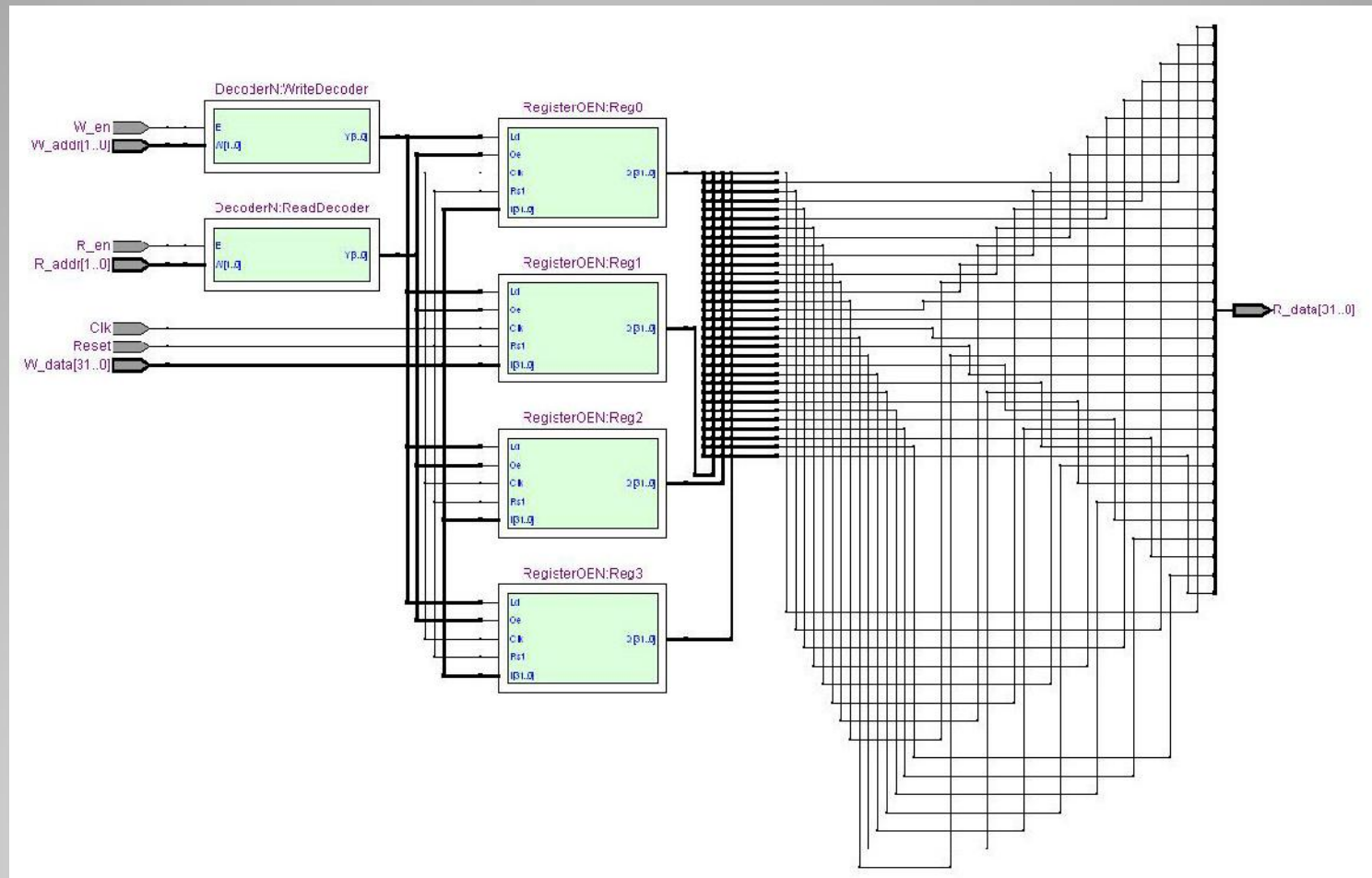

Register File (4 Reg X 32 Bits)

 


Register File (16 Reg X 16 Bits)

```
Fitter Status : Successful - Wed May 12 12:54:15 2010
Quartus II Version : 9.0 Build 132 02/25/2009 SJ Full Version
Revision Name : RegisterFile
Top-level Entity Name : RegisterFile
Family : Cyclone II
Device : EP2C35F672C6
Timing Models : Final
Total logic elements : 356 / 33,216 ( 1 % )
    Total combinational functions : 260 / 33,216 ( < 1 % )
    Dedicated logic registers : 256 / 33,216 ( < 1 % )
Total registers : 256
Total pins : 44 / 475 ( 9 % )
Total virtual pins : 0
Total memory bits : 0 / 483,840 ( 0 % )
Embedded Multiplier 9-bit elements : 0 / 70 ( 0 % )
Total PLLs : 0 / 4 ( 0 % )
```

Register File (16 Reg X 16 Bits)


Fit Summary

Our Programmable Processor's Datapath

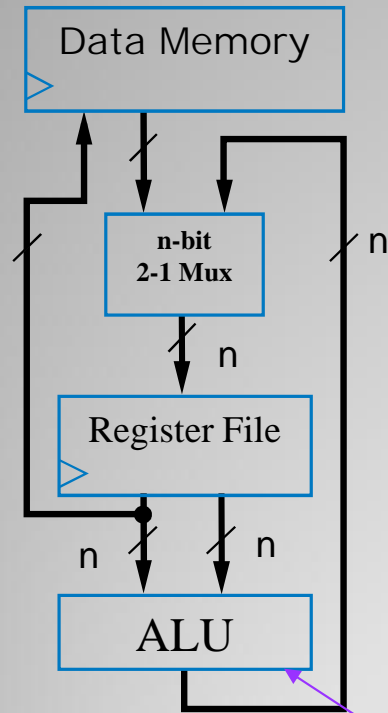


ALU has two inputs
fed by the Register File

 So, our Register File needs
two independent outputs.



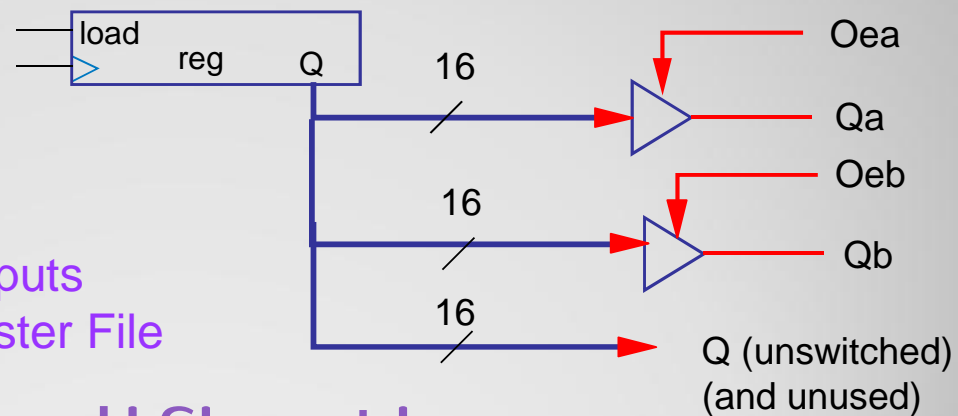We can accomplish this by adding a second
register output line, controlled by a second
output enable.



One More Modification

```
module RegisterDualOEN( I, Ld, Oea, Oeb, Clk, Rst, Qa, Qb );  
    parameter N = 16;  
    input [N-1:0] I;    // input data  
    input Oea;          // channel a output enable  
    input Oeb;          // channel b output enable  
    input Ld;           // register load enable  
    input Clk;          // input clock  
    input Rst;          // synchronous reset signal  
  
    output [N-1:0]Qa; // channel a output  
    output [N-1:0]Qb; // channel b output  
  
    // Your code goes here!
```

RegisterDualOEN

```

module RegisterFile( Clk, Rst, W_en, W_Addr, W_Data, Ra_Addr, Rb_Addr, Ra_en, Rb_en, Ra_Data, Rb_Data );
    input Clk;                                // system clock
    input Rst;                                // system reset
    input W_en;                               // write enable
    input [3:0] W_Addr;                       // write address
    input [15:0] W_Data;                      // data to write
    input [3:0] Ra_Addr, Rb_Addr;             // A side and B side read addresses
    input Ra_en, Rb_en;                      // A side and B side read enables

    output [15:0] Ra_Data, Rb_Data;           // A side and B side outputs (switched)
    output [15:0] RQ0;                       // Register 0 output (unswitched)

    wire [15:0] Ra_d , Rb_d; // read enables (decoder outputs)
    wire [15:0] W_d ;        // write enable (decoder output)
    wire [255:0] Q;          // holds the unswitched register outputs


    genvar I; // we are going to generate the registers

    // instantiate two read decoders and a write decoder
    GenericDecoder #(M(4)) WriteDecoder( W_Addr, W_en, W_d ); // write decoder
    GenericDecoder #(M(4)) ReadADecoder( Ra_Addr, Ra_en, Ra_d ); // A side read decoder
    GenericDecoder #(M(4)) ReadBDecoder( Rb_Addr, Rb_en, Rb_d ); // B side read decoder


    // instantiate the 16 dual-output registers
    generate
        for ( I=0; I<16; I=I+1 ) begin:rgen
            RegisterDualOE U( Clk, Rst, W_d[I], W_Data, Ra_d[I], Rb_d[I], Q[I*16+15:I*16], Ra_Data, Rb_Data );
        end
    endgenerate
endmodule

```

The Dual Output Register File

 

Register File with Dual Outputs

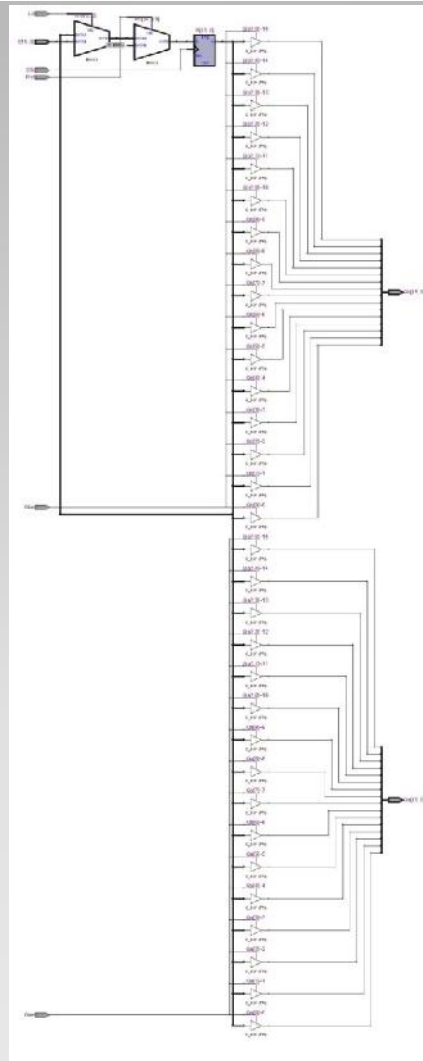

RegisterDualOE