

Verilog Lecture 4

- Using Procedures
- Simple Arithmetic Circuits
- Modular Design
- Vectors
- Constants
- Verification

```
module Mux2to1D( A, B, S, W )  
    input A, B, S;  
    output reg W;  
    // using a procedure  
    always @( A, B, S ) begin  
        if ( S ) W = B;  
        else W = A;  
    end  
endmodule
```

Mux2to1D.v

if-statement

```
if ( expression) begin
    // statements
end
```

if/else-statement

```
if ( expression) begin
    // statements
else begin
    // statements
end
```

case-statement

```
case ( expression )
    case_item: begin ... end
    case_item, case_item: begin ... end
    default: begin ... end
endcase
```

also: casez and casex which
we'll talk about later


for-loop : be very careful

```
for (initial_assignment; expression; step_assignment) begin
    // statements
end
```

Procedural Programming Statements

[BCD7seg.v](#)

BCD to 7-Seg Decoder

 

```
module TwoDecoder( I, D );
    input [1:0] I;
    output reg [3:0]D;

    always @( I ) begin
        if ( I == 2'd0 ) begin
            D = 4'b0001;
        end // I == 0
        else if ( I == 2'd1 ) begin
            D = 4'b0010;
        end // I == 1
        else if ( I == 2'd2 ) begin
            D = 4'b0100;
        end // I == 2
        else begin
            D = 4'b1000;
        end // I == 3 (default)
    end

endmodule
```

(To do: add Enable)

Decoder Example

```

always @ ( C )
  case ( C )
    4'h0: Display = 7'b00000001;
    4'h1: Display = 7'b10011111;
    4'h2: Display = 7'b...;
    4'h3: Display = 7'b...;
    4'h4: Display = 7'b...;
    4'h5: Display = 7'b...;
    4'h6: Display = 7'b..;
    4'h7: Display = 7'b...;
    4'h8: Display = 7'b...;
    4'h9: Display = 7'b0000100;
    default: Display = 7'b1111111; // blank
  endcase

```

```


module TwoDecoder( I, D );
  input [1:0] I;
  output reg [3:0]D;

  always @( I ) begin
    if ( I == 2'd0 ) begin
      D = 4'b0001;
    end // I == 0
    else if ( I == 2'd1 ) begin
      D = 4'b0010;
    end // I == 1
    else if ( I == 2'd2 ) begin
      D = 4'b0100;
    end // I == 2
    else begin
      D = 4'b1000;
    end // I == 3 (default)
  end

endmodule

```

Rewrite (Streamline) TwoDecoder

 

If NE is LOW the chip is enabled (normal operation). If NE is HIGH the chip is disabled and all outputs are 0

Using an 'if-else' statement add NE to your decoder.

```
if ( expression) begin
    // statements
else begin
    // statements
end
```

(Not) Enable

```
module Decoder( I, NE, D );
    input [1:0] I;    // inputs
    input NE;        // notEnable
    output reg [3:0] D; // outputs

    always @( I, NE ) begin
        if ( NE == 1'b1 )
            D = 4'b0;
        else begin
            D = 4'b0001 << I; // shift operator
        end // else

    end // always
endmodule
```

Yet Another Decoder Method


```

module Decoder( I, NE, D );
    parameter NAddr = 2; // default number of address lines

    input [NAddr-1:0] I; // address lines
    input NE;           // notEnable
    output reg [2**NAddr-1:0] D; // 2^NAddr decoder outputs

    always @( I, NE ) begin

        if ( NE == 1'b1 )
            D = 0; // truncation, but no warning
        else
            D = 1'b1 << I; // Verilog fills in with 0s, but no warning

    end // always
endmodule

```

Parameterized Version

```
module Decoder( I, NE, D );

    input [1:0] I;    // address lines
    input NE;        // notEnable

    output reg [3:0] D; // decoder outputs

    always @( I, NE ) begin
        D = 0;                // default output
        if ( NE == 0 ) begin // circuit is enabled
            D[I] = 1'b1;
        end // if
    end // always

endmodule
```

Last Version of Decoder

```

module Decoder( I, NE, D );
  parameter NAddr = 2;
  input [NAddr-1:0] I;
  input NE;
  output reg [2**NAddr-1:0] D;
  always @( I, NE ) begin
    if ( NE == 1'b1 )
      D = 0;
    else
      D = 1'b1 << I;
    end // always
endmodule

```

```

module Decoder( I, NE, D );

  input [1:0] I;    // address lines
  input NE;        // notEnable

  output reg [3:0] D; // decoder outputs

  always @( I, NE ) begin
    D = 0;          // default output
    if ( NE == 0 ) begin // circuit enabled
      D[I] = 1'b1;
    end // if
  end // always


endmodule

```


Parameterize This Version

		Carry	Sum
x	y	c	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

(b) Truth table


 


(c) Circuit

 



(d) Graphical symbol

Half Adder

  

```
module HalfAdd( input X, Y, output S, C );  
  
    assign S = X ^ Y;  
    assign C = X & Y;  
  
endmodule
```


Half Adder in Verilog

  

Half Adder RTL and Tech Map

c_i	x_i	y_i	c_{i+1}	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

(a) Truth table

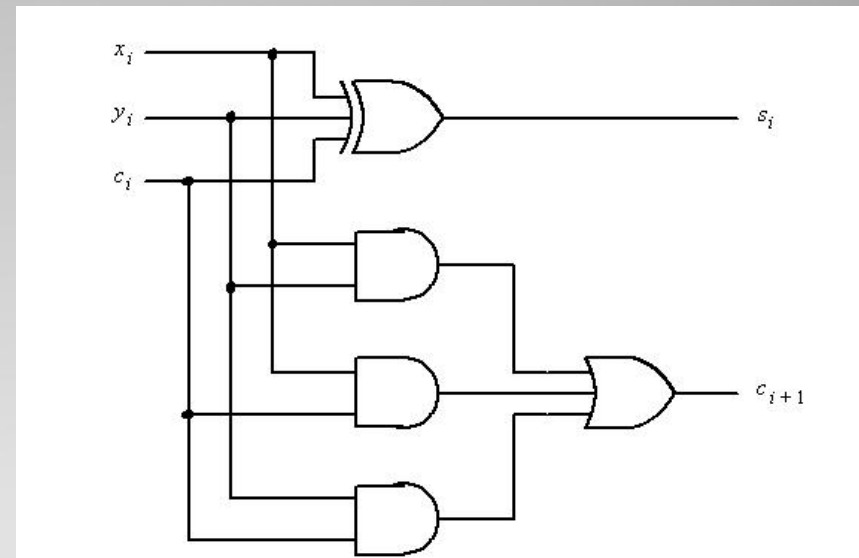

(c) Circuit

Full Adder

```
module FullAdd (Cin, X, Y, S, Cout);
```

```
  input Cin, X, Y;
```

```
  output S, Cout;
```

```
  wire Z1, Z2, Z3;
```

```
  xor ( S, X, Y, Cin );
```


```
  and ( Z1, X, Y );
```

```
  and ( Z2, X, Cin );
```


```
  and ( Z3, Y, Cin );
```

```
  or  ( Cout, Z1, Z2, Z3 );
```


```
endmodule
```

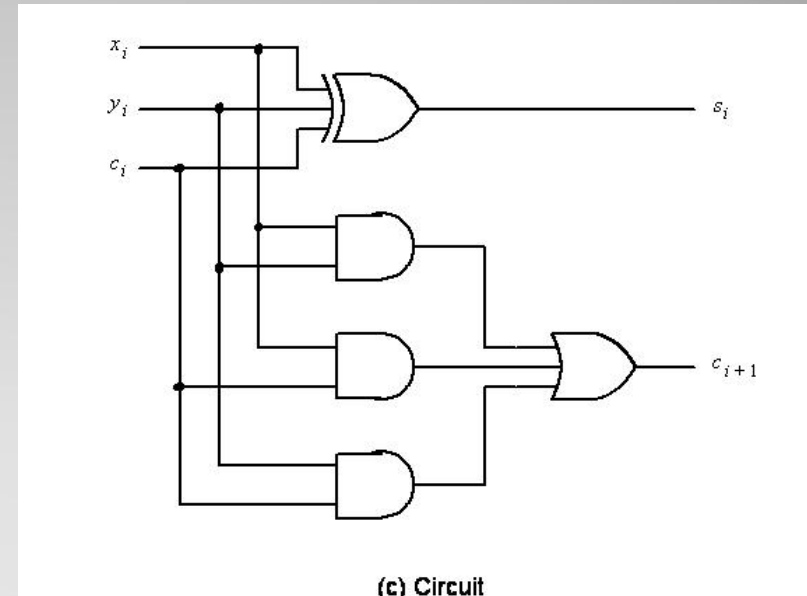

Full Adder in Structural Verilog

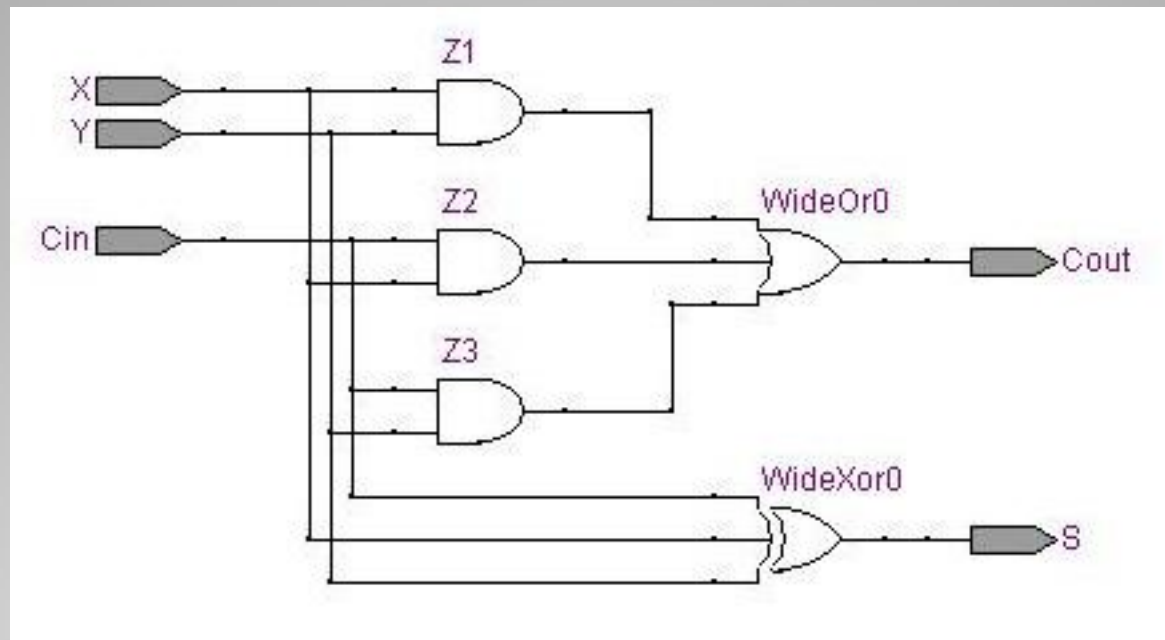

Full Adder From Netlist Viewer

 

(c) Circuit

```


module FullAdd( Cin, X, Y, S, Cout );
  input Cin, X, Y;
  output S, Cout;

  assign S = X ^ Y ^ Cin;
  assign Cout = (X & Y) | (X & Cin) | (Y & Cin);


endmodule

```

One Behavioral Version

 

Full Adder From Netlist Viewer


 


```
// module FullAdder( Cin, X, Y, S, Cout );
module FullAdd( input X, Y, output S, C );
    output S, Cout;
    assign S = X ^ Y;
    assign C1 = X & Y;

    HalfAdd H1( X, Y, S1, C1 );
    HalfAdd H2( Cin, S1, S, C2 );
    assign Cout = C1 | C2;

endmodule
```

Full Adder From Half Adders

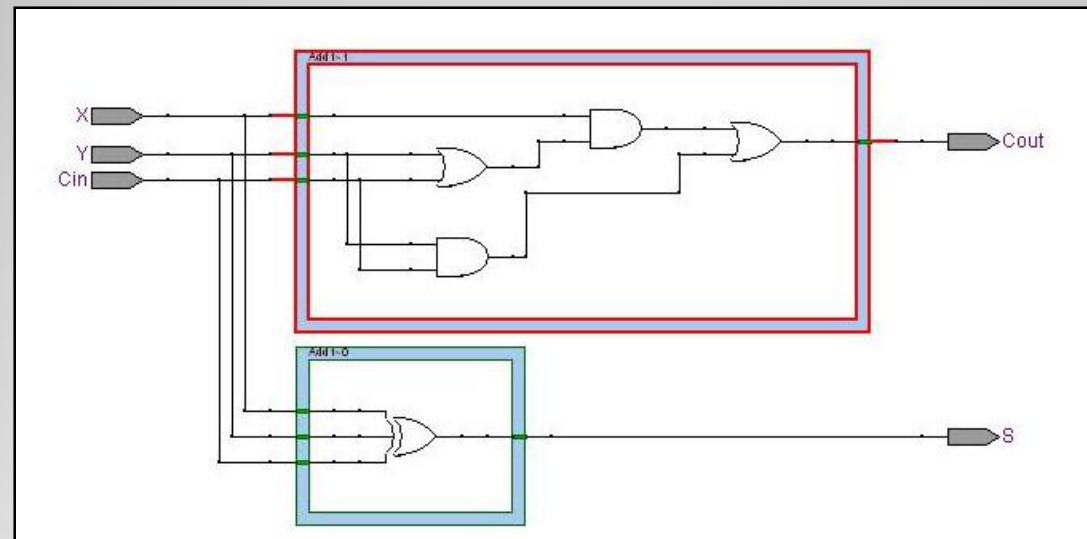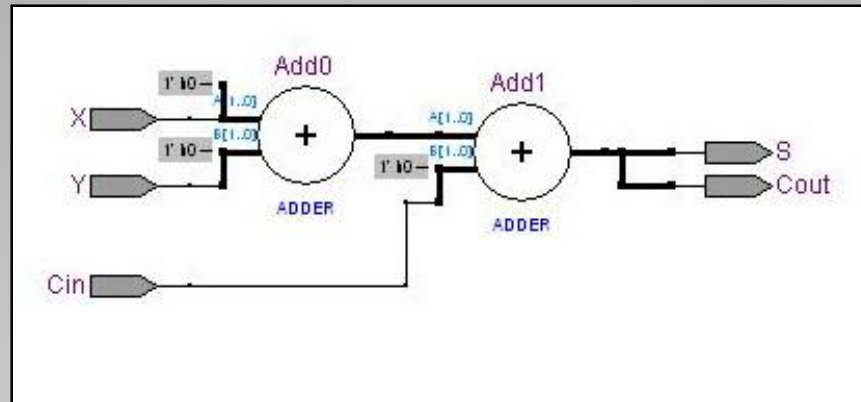

Full Adder From Netlist Viewer

```
// TCES 330
// 4/7/2010
// R. Gutmann
// This circuit implements a full adder
// using vector concatenation


module FullAdd( Cin, X, Y, S, Cout );
    input Cin, X, Y;
    output S, Cout;

    assign {Cout, S} = X + Y + Cin;

endmodule
```

Full Adder With Vector Notation

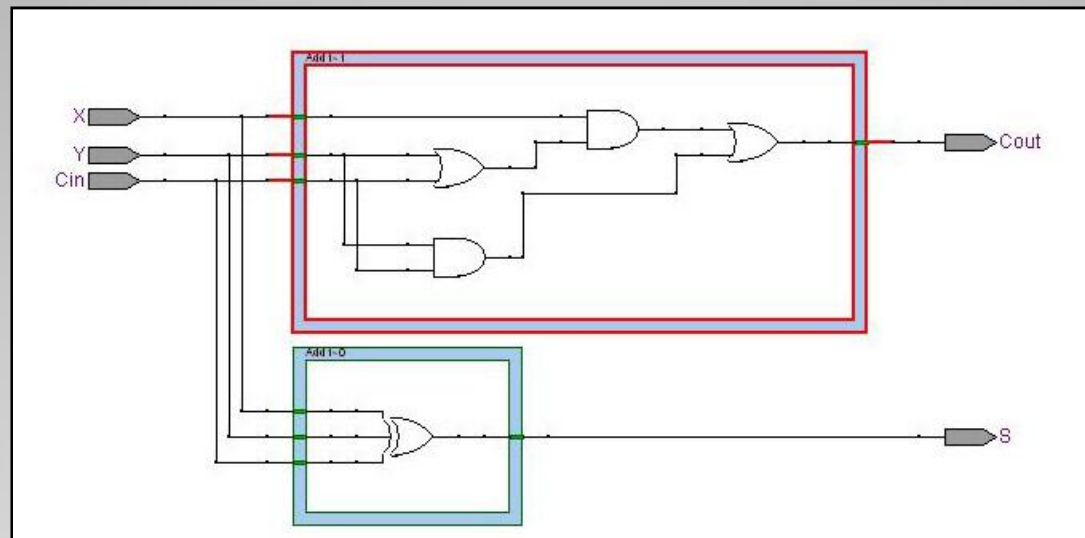- Looks the same as the last Netlist view.



Full Adder From Netlist Viewer

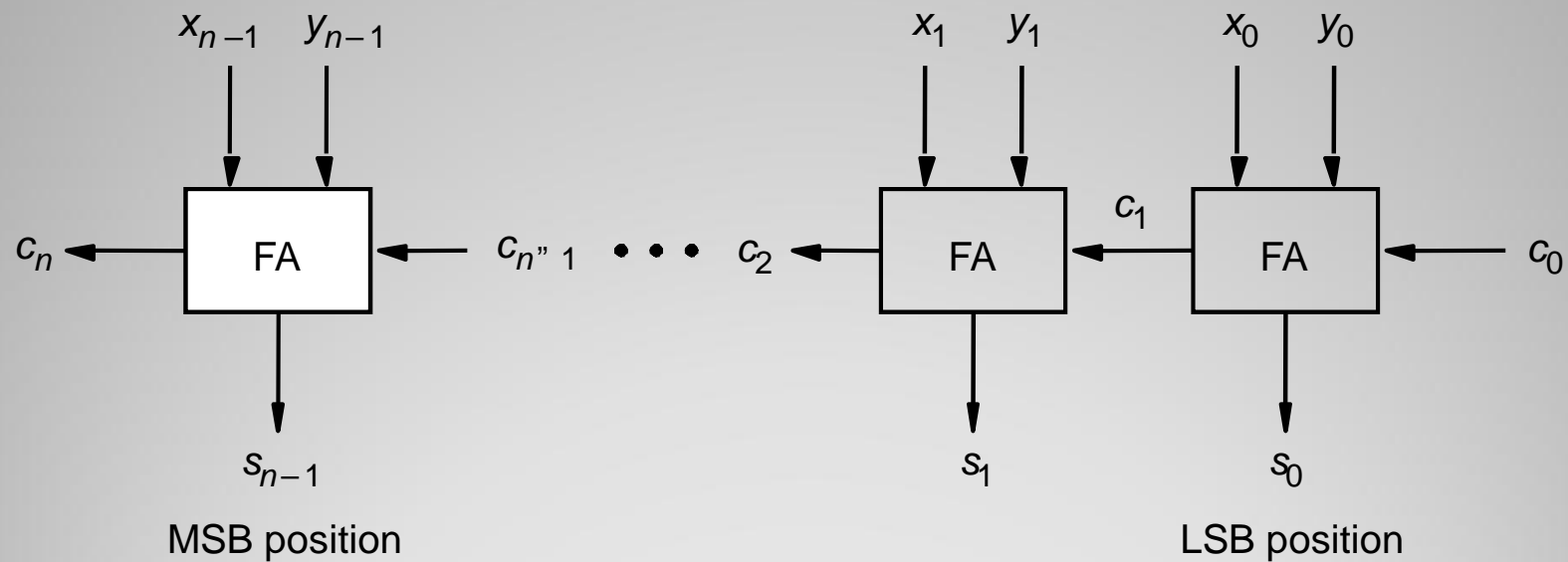


Figure 5.6. An n -bit ripple-carry adder.

Ripple-Carry Adder


```

module Adder4( Carryin, X3, X2, X1, X0, Y3, Y2, Y1, Y0,
                S3, S2, S1, S0, Carryout );
    input Carryin, X3, X2, X1, X0, Y3, Y2, Y1, Y0;
    output S3, S2, S1, S0, Carryout;
    wire C3,C2,C1;

    FullAdd Stage0 ( Carryin, X0, Y0, S0, C1 );
    FullAdd Stage1 ( C1, X1, Y1, S1, C2 );
    FullAdd Stage2 ( C2, X2, Y2, S2, C3 );
    FullAdd Stage3 ( C3, X3, Y3, S3, Carryout );

endmodule

module FullAdd ( Cin, X, Y, S, Cout );
    input Cin, X, Y;
    output S, Cout;
    assign S = X ^ Y ^ Cin,
    assign Cout = (X & Y) | (X & Cin) | (Y & Cin);


endmodule

```

Four-bit Ripple-Carry Adder

```
module Adder4( Carryin, X, Y, S, Carryout );  
  input  Carryin;  
  input  [3:0] X, Y;  
  output [3:0] S;  
  output Carryout;  
  wire   [3:1] C;  
  
  FullAdd Stage0 (Carryin, X[0], Y[0], S[0], C[1]);  
  FullAdd Stage1 (C[1], X[1], Y[1], S[1], C[2]);  
  FullAdd Stage2 (C[2], X[2], Y[2], S[2], C[3]);  
  FullAdd Stage3 (C[3], X[3], Y[3], S[3], Carryout);  
  
endmodule
```

Same Adder Using Vectors

 

- Real gates have some delay
Outputs don't change immediately after inputs change

Additional Considerations

Non-Ideal Gate Behavior -- Delay

```
module Adder4( Carryin, X, Y, S, Carryout );  
  
    input  Carryin;  
    input  [3:0] X, Y;    // addends  
  
    output [3:0] S;        // sum  
    output Carryout;  
  
    assign {Carryout, S} = X + Y + Carryin;  
  
endmodule
```

How We Would Really Do It

```
module AdderN( Carryin, X, Y, S, Carryout );  
    parameter N = 8;  
    input  Carryin;  
    input  [N-1:0] X, Y; // addends  
  
    output [N-1:0] S;      // sum  
    output Carryout;  
  
    assign {Carryout, S} = X + Y + Carryin;  
  
endmodule
```

How We Would Really Really Do It

```
// TCES 330
// 04/07/2010
// R. Gutmann
// This circuit adds 5 to X (eight bits)
// and outputs the sum S (eight bits) plus overflow flag

module Add5To( X, S, Overflow );
    input  [7:0] X;  // eight bits of input
    output [7:0] S;  // eight bits of output
    output Overflow;

    AdderN #(.N(8)) U1( 1'b0, X, 8'h5, S, Overflow );
endmodule
```

Example Using Constants

```

module BCD7seg( C, Display );
    input      [3:0] C;          // input code
    output reg [0:6] Display;    // seven-segment display output
    // Note: a '0' turns the segment ON
    // Note: Segment 6 is in the right most bit, below
    always @ ( C )
        if ( C == 4'h0 )
            Display = 7'b0000001;
        else if ( C == 4'h1 )
            Display = 7'b ...
        else if ( C == 4'h2 )
            Display = 7'b ...
        else if ( C == 4'h3 )
            Display = 7'b ...
        else if ( C == 4'h4 )
            Display = 7'b ...
        else if ( C == 4'h5 )
            Display = 7'b ...
        else if ( C == 4'h6 )
            Display = 7'b ...
        else if ( C == 4'h7 )
            Display = 7'b ...
        else if ( C == 4'h8 )
            Display = 7'b ...
        else if ( C == 4'h9 )
            Display = 7'b ...
        else
            Display = 7'b1111111; // blank
endmodule

```

Constants + Procedure + if

```

module BCD7seg( C, Display );
  input      [3:0] C;          // input code
  output reg [0:6] Display;    // seven-segment display output
  // Note: a '0' turns the segment ON
  // Note: Segment 6 is in the right most bit, below
  always @ ( C )
    case ( C )
      4'h0: Display = 7'b0000001;
      4'h1: Display = 7'b ...
      4'h2: Display = 7'b ...
      4'h3: Display = 7'b ...
      4'h4: Display = 7'b ...
      4'h5: Display = 7'b ...
      4'h6: Display = 7'b ...
      4'h7: Display = 7'b ...
      4'h8: Display = 7'b ...
      4'h9: Display = 7'b ...
      default: Display = 7'b1111111; // blank
    endcase
endmodule

```

Constants + Procedure + case

Question:

How do we know it works?

- All of this design in Verilog is well and good, but how do we know if we got it right?
- We need to test or verify the design.
- Traditional Verilog testing techniques are not supported by Quartus II (its purpose is to synthesize circuits).
- However, we can test using ModelSim.

Verification