


# More Verilog Constructs

ModelSim  
Parameters  
Procedures

ModelSim

- We will use ModelSim to simulate (test) some of our circuit designs.
- We will generate test signal waveforms similar to those used in the QSim example, except we'll generate the waveforms programmatically rather than graphically.
- The programming language we'll use in ModelSim is Verilog.
- We'll need to learn just a handful of new Verilog constructs.

## ModelSim

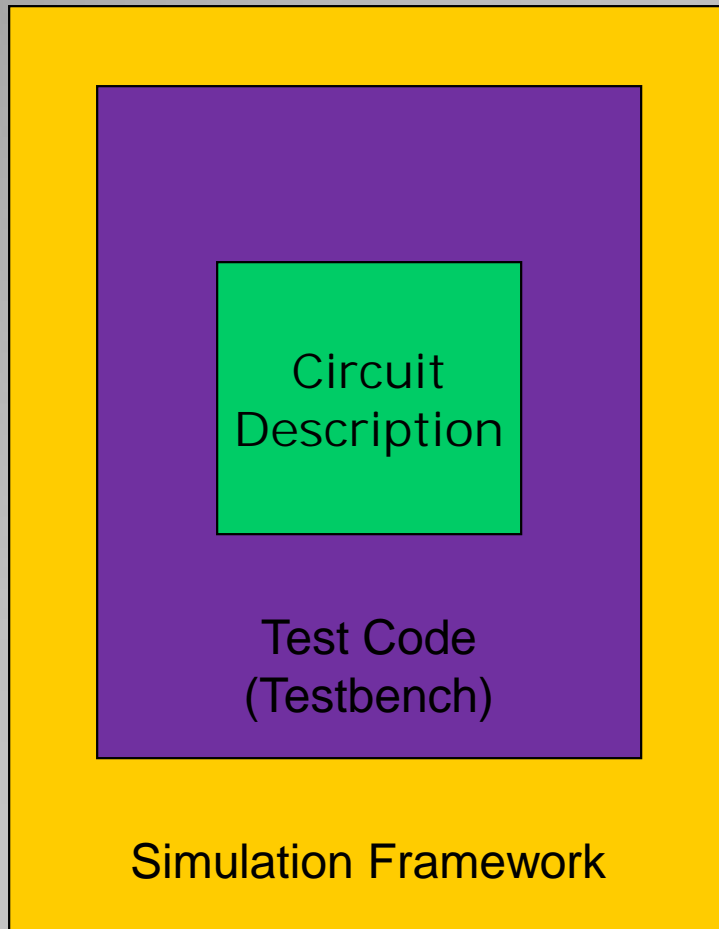

Circuit Description defines

- Circuit inputs
- Circuit outputs
- Circuit Elements (gates)
- Connections between gates

Testbench defines

- Test signals input to circuit
- What to do with circuit outputs

Simulation Framework

- Provides a place for the simulation to 'live'
- Support services such as I/O
- Provides support elements such as basic gate types

## Elements of a Simulation

```

`timescale 1ns/1ns // defines unit of time
module test_light; // note: no I/O ports
    reg [1:0] Input;
    wire GreenLED;

    light dut( Input[0], Input[1], GreenLED ); // module
    initial // Test stimulus
        begin
            Input = 2'h0;
            #20 Input = 2'h1;
            #20 Input = 2'h3;
            #20 Input = 2'h2;
        end

    initial
        $monitor( $stime,, Input,, GreenLED );

endmodule

```

## Testbench for 'light' module

- ' timescale defines what one unit of time is.
- 'initial' is like 'always' except it runs only once at the beginning of the simulation – so it doesn't require a sensitivity list to tell it when to run.
- #20 means "wait for 20 clock ticks before you do anything else in this procedure." Of course 20 could be any positive integer.
- \$monitor(args) prints out a line of text whenever any of its arguments changes.
- \$stime stands for 'simulation time'.

Refer to [Sutherland](#)

## New Verilog Elements

`' timescale time_unit base / precision base`

Specifies the time units and precision for delays:

- 

`time_unit` is the amount of time a delay of 1 represents. The time unit must be 1, 10, or 100

- 

`base` is the time base for each unit, ranging from seconds to femtoseconds, and must be:

s ms us ns ps or fs

- 

`precision` and `base` represent how many decimal points of precision to use relative to the time units.

Example: ``timescale 1 ns / 10 ps`

Indicates delays are in 1 nanosecond units with 2 decimal points of precision (10 ps is .01 ns).

Note: There is no default timescale in Verilog; delays are simply relative numbers until a timescale directive declares the units and base the numbers represent.

From Sutherland's Verilog Reference Guide

## The `' timescale` Directive

Moving ON



Consider:

```
module NANDn( I, W );  
    parameter n = 8;  
    input [n-1:0] I;  
    output W = ~&I;  
endmodule
```

```
module NANDnTest( Z );  
    output Z;  
  
    wire [15:0] I = 16'd255;  
    NANDn #(.n(16)) U1( I, Z );  
  
endmodule
```

# NANDn

## Recall:

```
module Mux2to1D( A, B, S, W );  
  input A, B, S;  
  output reg W; // register variable W  
  
  // using a procedure  
  always @( A, B, S ) begin  
    if ( S ) W = B; // blocking  
    else W = A;  
  end  
endmodule
```

Changes inside  
the procedure

Sensitivity List

begin/end block

Blocking assignment

if/else statement

# Procedure Example

- Net data types

**wire** : is the type we'll mostly use  
there are about 10 more mostly dealing with 'wired'  
ANDs and ORs

- Variable data types

Used for programming storage in procedural blocks

**reg** : a variable of any bit size; unsigned unless  
explicitly declared as signed

**integer** : a signed 32-bit variable (we'll use these in  
'for' loops)

**genvar** : used in generate blocks (otherwise, like  
'integer')

**time, real, realtime** : don't synthesize

## Verilog Data Types

- Other data types

- parameter**

- we used a parameter in NANDn

- localparam**

- like parameter, but can't be directly redefined from outside the module
    - we'll use these in state machine to give names to states.

- Refer to the Quick Reference Guide

Verilog Data Types, cont.

- **initial** blocks

Process statements one time only

Used in testbench design

- **always** blocks

An infinite loop

Use sensitivity list to determine when to execute the block

Use begin/end to delineate

## Procedure Blocks

- `always @( A, B, C )`  
implies combinational logic  
block runs whenever A or B or C changes  
also written `(A or B or C)`
- `always @*`  
implies combinational logic  
block runs whenever any variable read within the block changes  
new in Verilog 2001
- `always @( posedge ClkA, negedge ClkB )`  
implies sequential logic  
block runs if ClkA sees a positive edge or if ClkB sees a negative edge  
a specific edge should be specified for each signal in the list
- Don't mix combinational and sequential sensitivity lists

## Sensitivity Lists

- `A = B;`

Blocking assignment

Expression is evaluated and assigned when the statement is encountered.

In `begin M=N; N=M; end` the first assignment changes M before the second one reads it.

- `A <= B;`

Non-blocking assignment

Expression is evaluated when the statement is encountered and assignment is postponed until the end of the `begin/end` block.

In `begin M<=N; N<=M; end` both assignments will be evaluated before M or N changes (swaps values).

## Procedural Assignment Statements

- Use blocking assignments ( $=$ ) to model combinational logic.
- Use non-blocking assignments ( $<=$ ) to model sequential logic.
- This helps avoid race conditions that can develop.

Blocking/Non-blocking Uses



### if-statement

```
if ( expression) begin
    // statements
end
```

### if/else-statement

```
if ( expression) begin
    // statements
else begin
    // statements
end
```

### case-statement

```
case ( expression)
    case_item: begin ... end
    case_item, case_item: begin ... end
    default: begin ... end
endcase
```

also: casez and casex which  
we'll talk about later

for-loop : be very careful

```
for (initial_assignment; expression; step_assignment) begin
    // statements
end
```

# Procedural Programming Statements

- May or may not synthesize:

`while (expression)`

`repeat (number)`

`forever`

`disable group_name`

Procedural Programming  
Statements, cont.

From Lab 1, Part II:

```
module Mux8( S, X, Y, M );
    input S;                // mux select line in
    input  [7:0] X, Y;      // mux inputs
    output [7:0] M;         // mux output

    // the mux:
    assign M[0] = (~S & X[0]) | (S & Y[0]);
    assign M[1] = (~S & X[1]) | (S & Y[1]);
    assign M[2] = (~S & X[2]) | (S & Y[2]);
    assign M[3] = (~S & X[3]) | (S & Y[3]);
    assign M[4] = (~S & X[4]) | (S & Y[4]);
    assign M[5] = (~S & X[5]) | (S & Y[5]);
    assign M[6] = (~S & X[6]) | (S & Y[6]);
    assign M[7] = (~S & X[7]) | (S & Y[7]);

endmodule
```

## Mux8 Example

```

module Mux8( S, X, Y, M );
    input S;                // mux select line in
    input  [7:0] X, Y;      // mux inputs
    output reg [7:0] M;     // mux output

    integer i;
    always @ ( S, X, Y ) begin
        for ( i=0; i<8; i=i+1 ) begin
            M[i] = (~S & X[i]) | (S & Y[i]);
        end // for-loop
    end // always
endmodule

```

Mux8, for-loop

```

module MuxN( S, X, Y, M );
    parameter N = 8;
    input S;                // mux select line in
    input  [N-1:0] X, Y;    // mux inputs
    output reg [N-1:0] M;   // mux output

    integer i;
    always @ ( S, X, Y ) begin
        for (i=0; i<N; i=i+1) begin
            M[i] = (~S & X[i]) | (S & Y[i]);
        end // for-loop
    end // always

endmodule

```

## MuxN: More Versatile

```
module MuxNTest( S, X, Y, M );  
    localparam Width = 32;  
    input S;                      // mux select line in  
    input  [Width-1:0] X, Y;      // mux inputs  
    output [Width-1:0] M;         // mux output  
  
    MuxN #(.N(Width)) U1( S, X, Y, M );  
  
endmodule
```

MuxNTest : Sets N

We want to build a circuit that has eight inputs ( $x_7, x_6, \dots, x_0$ ) and produces an output of  $F = 1$  if there are at least three consecutive ones in the input; otherwise output  $F = 0$ . So if  $X = 00111100$  the output would be  $F = 1$ , but if  $X = 10101010$  the output would be  $F = 0$ .

The truth table for  $F$  would have 256 entries – too long for us to deal with easily.

On the other hand, we can see that

$$F = x_0x_1x_2 + x_1x_2x_3 + x_2x_3x_4 + x_3x_4x_5 + x_4x_5x_6 + x_5x_6x_7$$

Write a Verilog module that computes  $F$ :

```
module ThreeOnes( X, F );  
    input [7:0] X;  
    output F;  
    ...  
endmodule
```

## Three Ones Circuit

Now what if I said that X has 32 elements?

It wouldn't be very much fun writing out F, would it?

But we can use a for-loop and an if-statement to implement F.

- These statements must be in a procedure
- F must be declared as a reg (since it will be computed in a procedure)
- We might as well make the size of X a parameter (N)
- The procedure is going to look something like this:

```
integer I;  
always @ ( ) begin  
    F = 0;    // default value  
    for ( I=0; ...; I=I+1 ) begin  
        if ( X[I] & X[I+1] & X[I+2] ) F = 1;  
    end // for-loop  
end // always
```

## Three Ones Circuit, cont.



```

module ThreeOnes( X, F );
    parameter N = 8;
    input [N-1:0] X;
    output reg F;

    integer I;


    always @* begin
        F = 0;
        for ( I=0; I<N-2; I=I+1 )
            F = F | X[I]&X[I+1]&X[I+2];
    end

    /*always @ ( X ) begin
        F = 0;
        for ( I=0; I<N-2; I=I+1 )
            if ( X[I]&X[I+1]&X[I+2] ) F = 1;
    end*/

endmodule

```

ThreeOnes.v

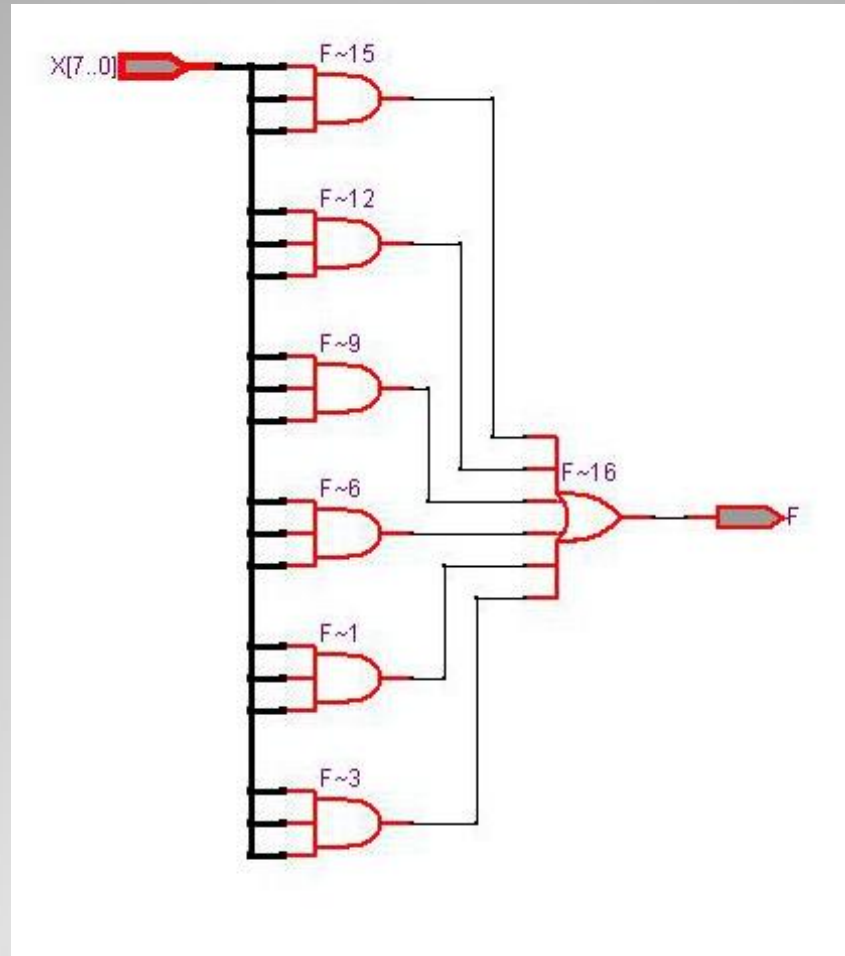

Three Ones Circuit (RTL)

- Test Add5To module
- Test ThreeOnes module

Using for-loop in a Testbench

```
module CountOnes( X, F );  
    input [15:0] X;  
    output reg [3:0] F;  
  
    integer I;  
  
    always @* begin  
        F = 0;  
        for ( I=0; I<16; I=I+1 )  
            if ( X[I] == 1'b1 )  
                F = F + 1'b1;  
        end  
    endmodule
```

## Count Ones

- for-loop example
- generate-loop example
- Arithmetic statements

## Chapter 5 Verilog Examples

```

module adder4( carryin, x3, x2, x1, x0, y3, y2, y1, y0,
               s3, s2, s1, s0, carryout );
    input carryin, x3, x2, x1, x0, y3, y2, y1, y0;
    output s3, s2, s1, s0, carryout;
    wire c3,c2,c1;

    fulladd stage0 ( carryin, x0, y0, s0, c1 );
    fulladd stage1 ( c1, x1, y1, s1, c2 );
    fulladd stage2 ( c2, x2, y2, s2, c3 );
    fulladd stage3 ( c3, x3, y3, s3, carryout );

endmodule

module fulladd ( Cin, x, y, s, Cout );
    input Cin, x, y;
    output s, Cout;
    assign s = x ^ y ^ Cin,
    assign Cout = (x & y) | (x & Cin) | (y & Cin);

endmodule

```

# Recall: Ripple-Carry Adder

```
module adder4( carryin, x3, x2, x1, x0, y3, y2, y1, y0,  
               s3, s2, s1, s0, carryout );  
input carryin, x3, x2, x1, x0, y3, y2, y1, y0;  
output s3, s2, s1, s0, carryout;  
wire c4,c3,c2,c1,c0;  
assign c0 = carryin;  
assign carryout = c4;
```


```
//fulladd stage0 ( c0, x0, y0, s0, c1 );  
//fulladd stage1 ( c1, x1, y1, s1, c2 );  
//fulladd stage2 ( c2, x2, y2, s2, c3 );  
//fulladd stage3 ( c3, x3, y3, s3, c4 );
```

```
// something like:  
  for (i=0; i<4; i++) begin  
    fulladd stagei( ci, xi, yi, si, ci+1 )  
  end
```

```
endmodule
```

We can't instantiate a  
module within a for-loop

## What We Would Like to Do

 

(c) Circuit

```

module FullAdd( Cin, X, Y, S, Cout );
  input Cin, X, Y;
  output S, Cout;

  assign S = X ^ Y ^ Cin;
  assign Cout = (X & Y) | (X & Cin) | (Y & Cin);

endmodule

```

## Behavioral Version of Full Adder



We can do this:

```
module addern (carryin, X, Y, S, carryout);
  parameter n=32;
  input carryin;
  input [n-1:0] X, Y;
  output reg [n-1:0] S; // value assigned in always block
  output reg carryout; // value assigned in always block
  reg [n:0] C;          // notice the size of C
  integer k;           // used as for-loop index

  always @(X, Y, carryin) begin
    C[0] = carryin; // note use of blocking assignments
    for (k = 0; k < n; k = k+1) begin
      S[k] = X[k] ^ Y[k] ^ C[k]; // we unwrap 'fulladd'
      C[k+1] = (X[k] & Y[k]) | (X[k] & C[k]) | (Y[k] & C[k]);
    end
    carryout = C[n];
  end // always

endmodule
```

addern (Figure 5.28)


```

module ripple_g( carryin, X, Y, S, carryout );
  parameter n = 4;
  input carryin;
  input [n-1:0] X, Y;
  output [n-1:0] S;
  output carryout;
  wire [n:0] C;

  genvar i; // new
  assign C[0] = carryin;
  assign carryout = C[n];
  generate // kind of like a procedure block
    for ( i = 0; i <= n; i = i+1 )
      begin:addbit // notice we name the block
        fulladd stage( C[i], X[i], Y[i], S[i], C[i+1] );
      end
  endgenerate
endmodule

```

adder Using 'generate'

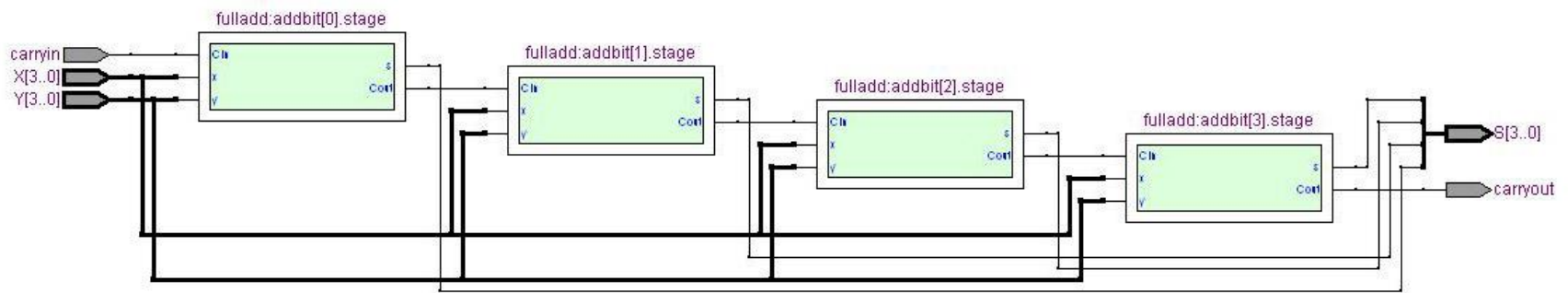

What Quartus II Synthesized