

 


TCES 330

Processors

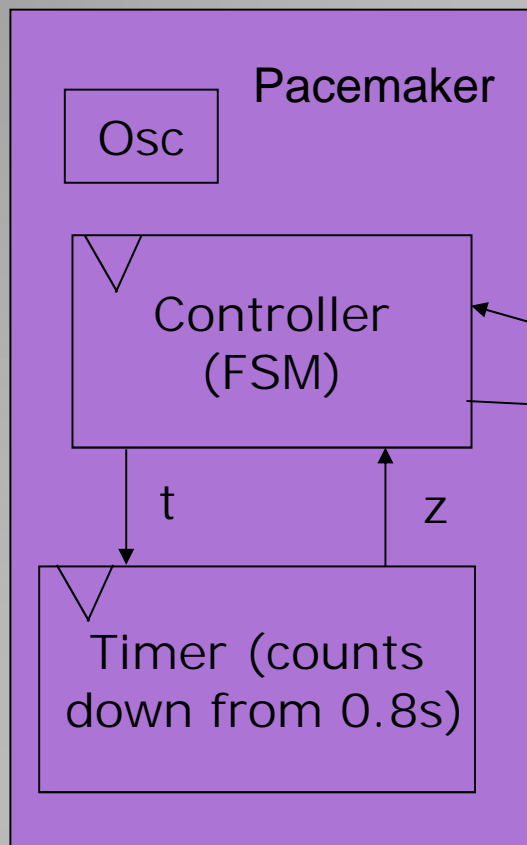

 
s: sense (contract.)  
 p: pulse (pace)  
 t: reset timer  
 z: timer at zero



# Pacemaker is a Processor


Recall:

Inputs:  $b$ ; Outputs:  $x$

 


Laser is ON for three clock ticks

 But what if we needed the laser to stay on, 16 or 256 clock cycles?




Maybe not

Recall the Laser Surgery FSM

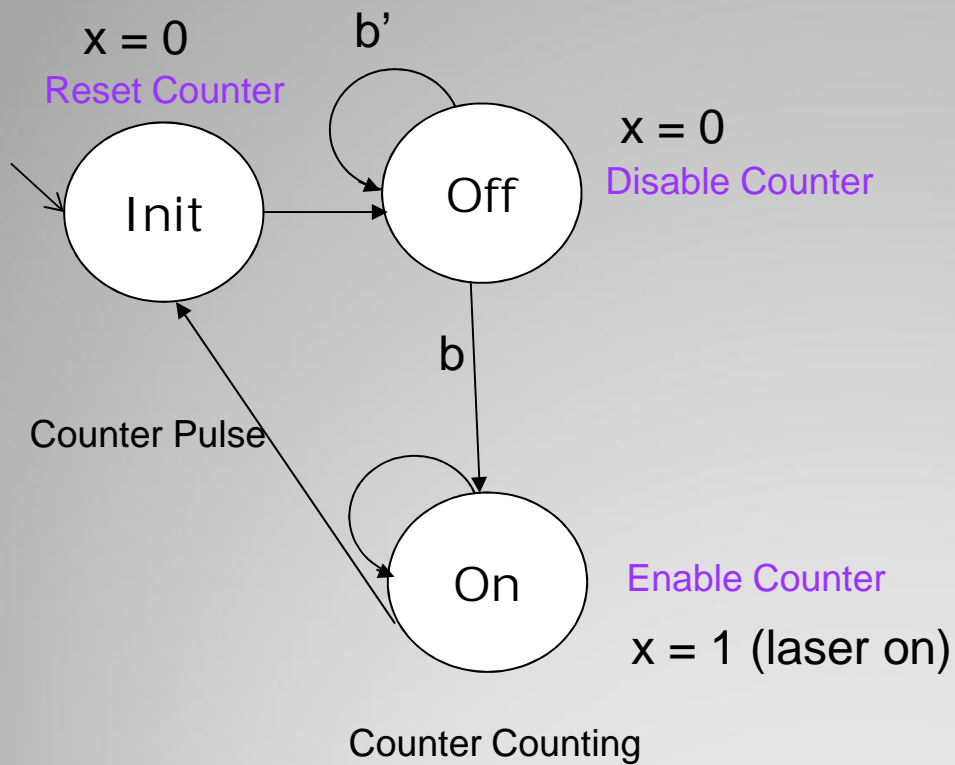


- Add a **counter** that we enable in the On State
- When the counter pulses at the desired count, we change state

## Laser FSM Using Datapath

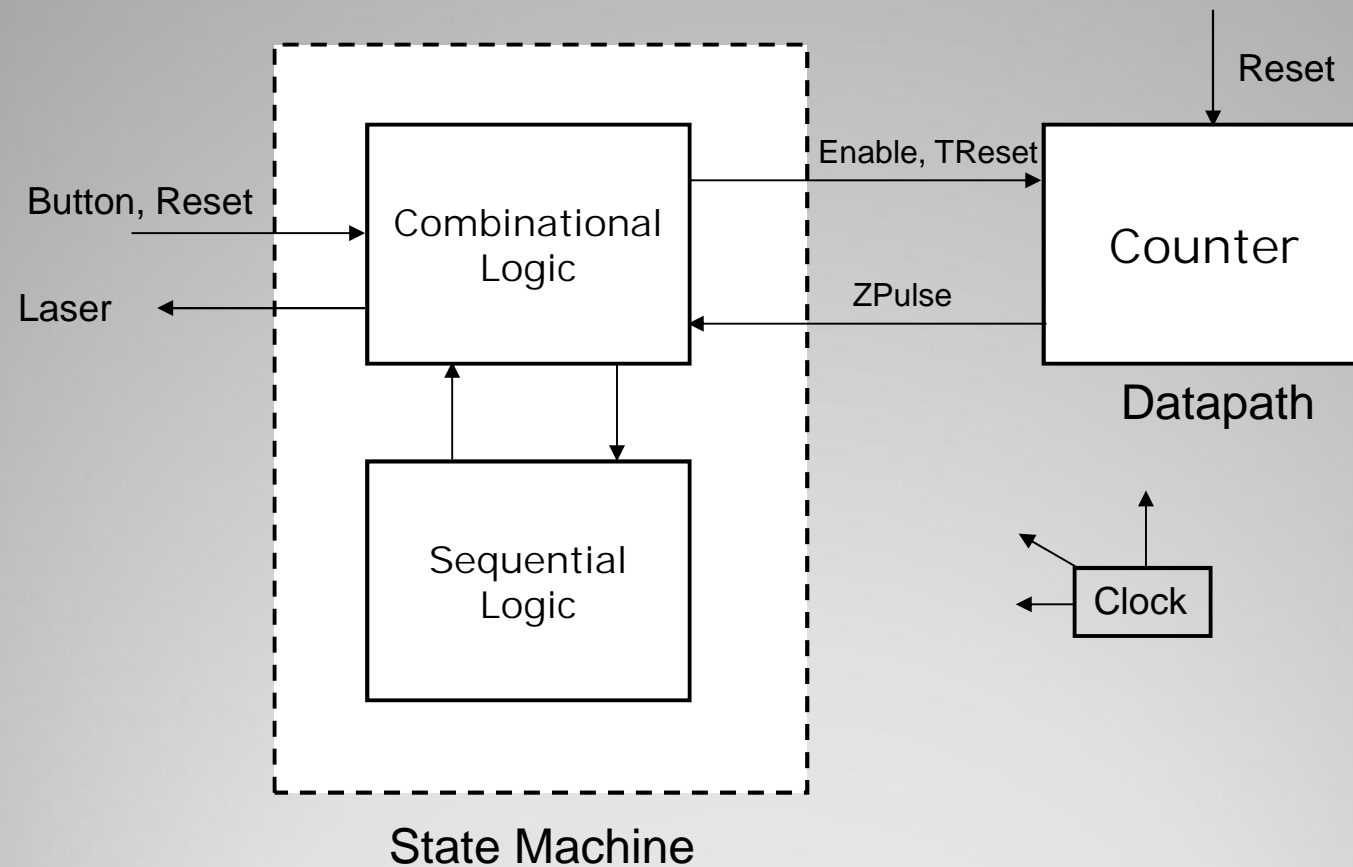

Note: This looks a lot like the *Pacemaker* project

# Laser Processor Block Diagram

 


- Example of how to create a high-level state machine to describe desired processor behavior
- Laser-based distance measurement – pulse laser, measure time T to sense reflection

Laser light travels at speed of light,  $3 \cdot 10^8 \text{ m/sec}$


Distance is thus  $D = T \text{ sec} * 3 \cdot 10^8 \text{ m/sec} / 2$

From F. Vahid's *Digital Design*

## Laser Ranging System


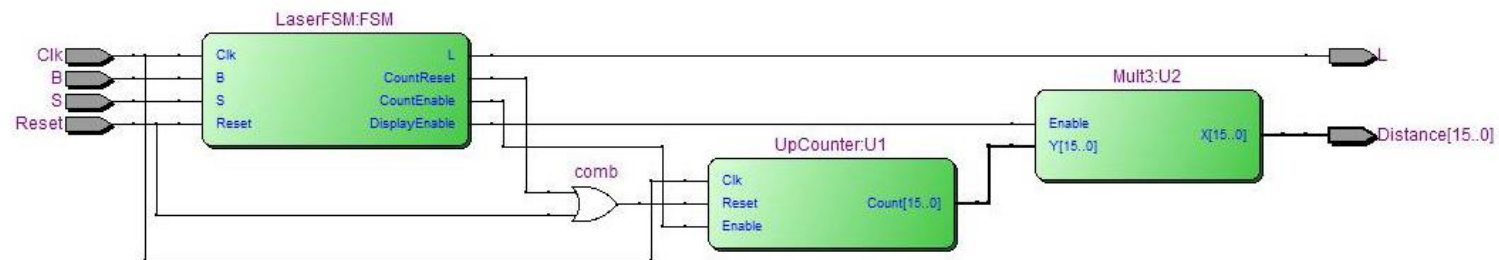


Laser Ranger Block Diagram

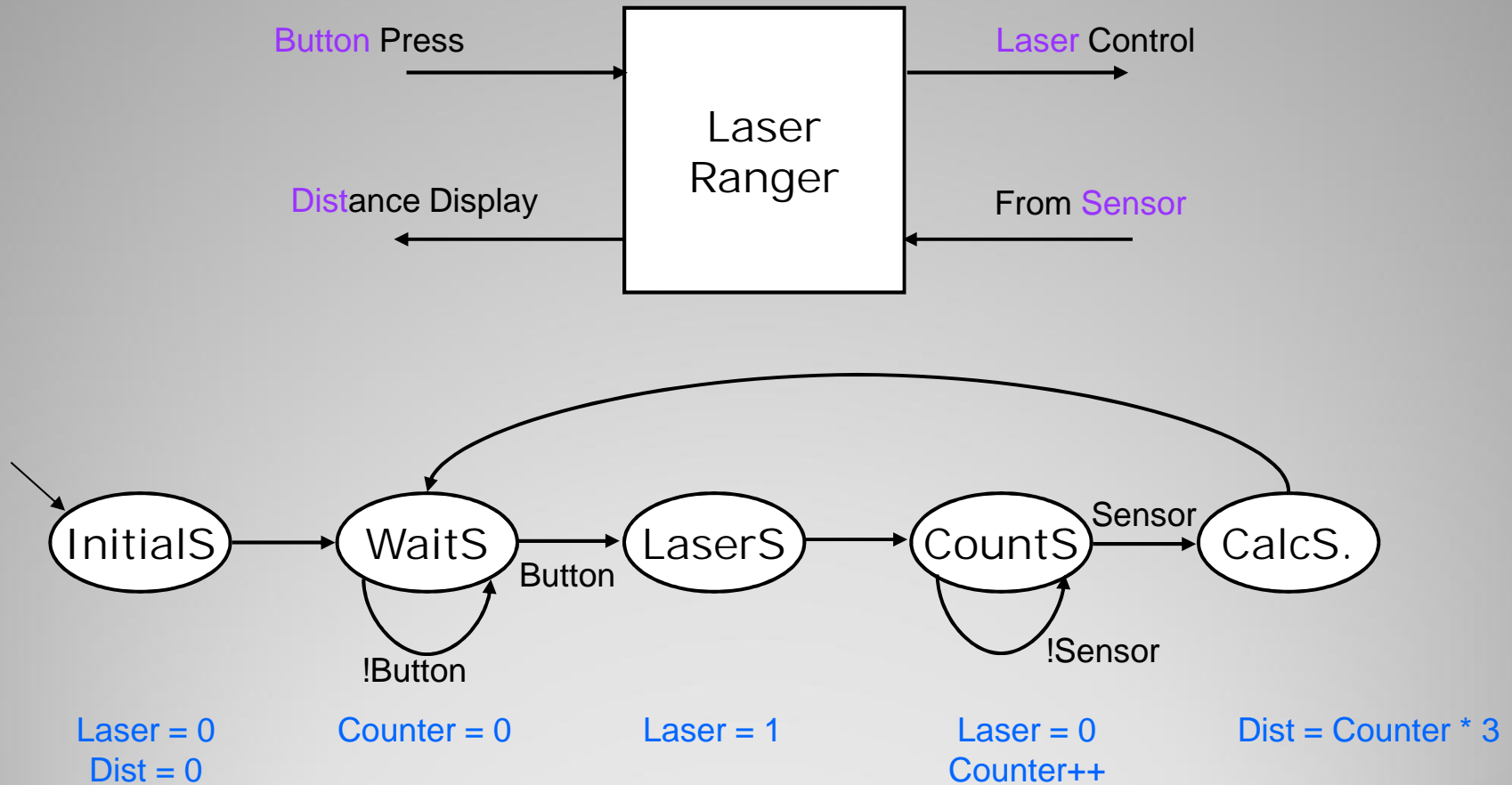
  
# High Level State Machine For Laser Ranger






- Four possible display items  
 Temperature (T), Average miles-per-gallon (A), Instantaneous mpg (I), and Miles remaining (M) -- each is 8-bits wide  
 Choose which to display using two inputs x and y  
 Could Use 8-bit 4x1 mux

From F. Vahid


## N-bit Mux Example

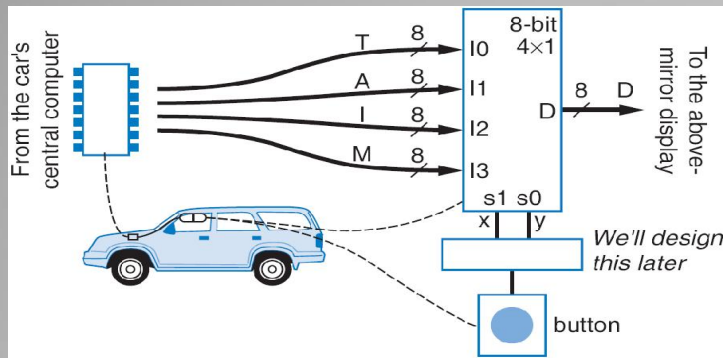

- Recall: Four simultaneous values from car's computer
- To reduce wires: Computer writes only 1 value at a time, loads into one of four registers

Was:  $8+8+8+8 = 32$  wires

Now:  $8 + 2 + 1 = 11$  wires

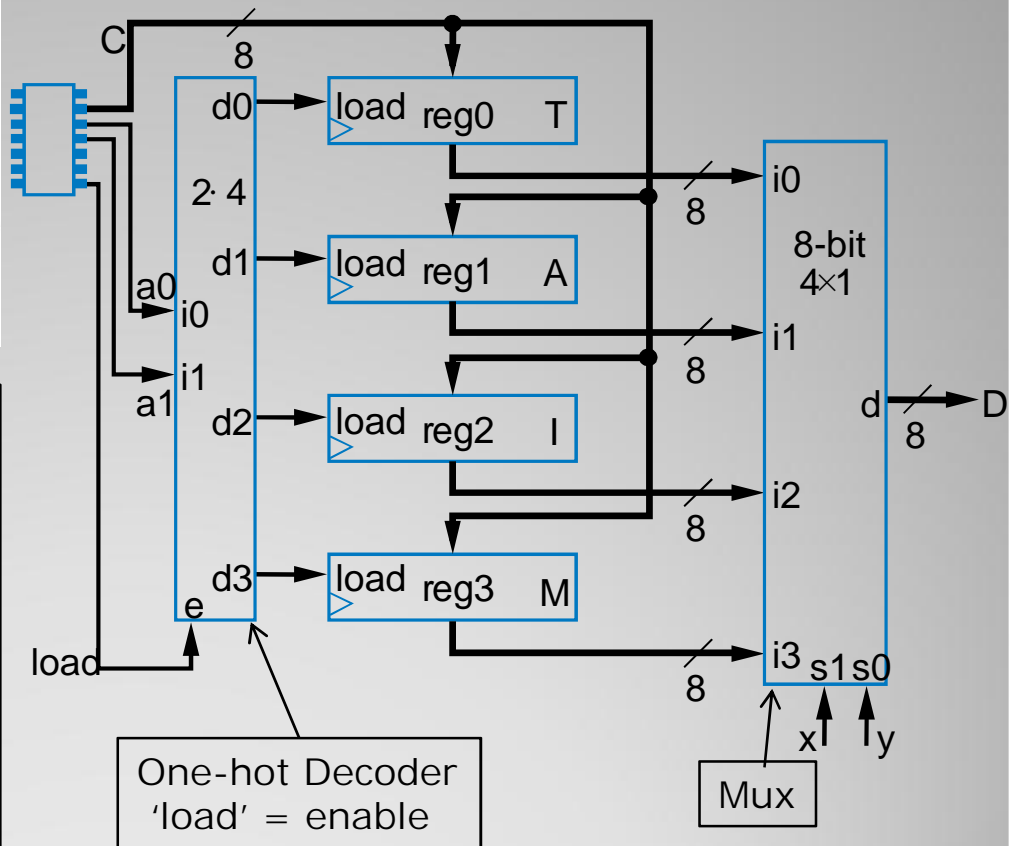

## Register Example: Above-Mirror Display

From F. Vahid

```

module MirrorDisplay( C, A, Load, Clock, S, D );
  input [7:0] C; // data from microprocessor
  input [1:0] A; // data key (T=0, A=1, I=2, M=3)
  input Load;    // data ready signal from micro
  input Clock;   // our system clock
  input [1:0] S; // users selection (what to display)
  output [7:0] D; // data to display (we don't worry about how)
  wire [3:0] RD;  // decoder output

  DecoderN #(.N(2)) U0( A, Load, RD ); // 2 address lines


  wire [7:0] I3, I2, I1, I0; // register outputs, mux inputs
  // the registers:
  PLoadRegN #(.N(8)) R0( C, RD[0], Clock, I0 ); // T-register
  PLoadRegN #(.N(8)) R1( C, RD[1], Clock, I1 ); // A-register
  PLoadRegN #(.N(8)) R2( C, RD[2], Clock, I2 ); // I-register
  PLoadRegN #(.N(8)) R3( C, RD[3], Clock, I3 ); // M-register

  // the mux:
  MuxNw4_1 #(.N(8)) M0( S, I0, I1, I2, I3, D );

endmodule

```

## Mirror Display Verilog

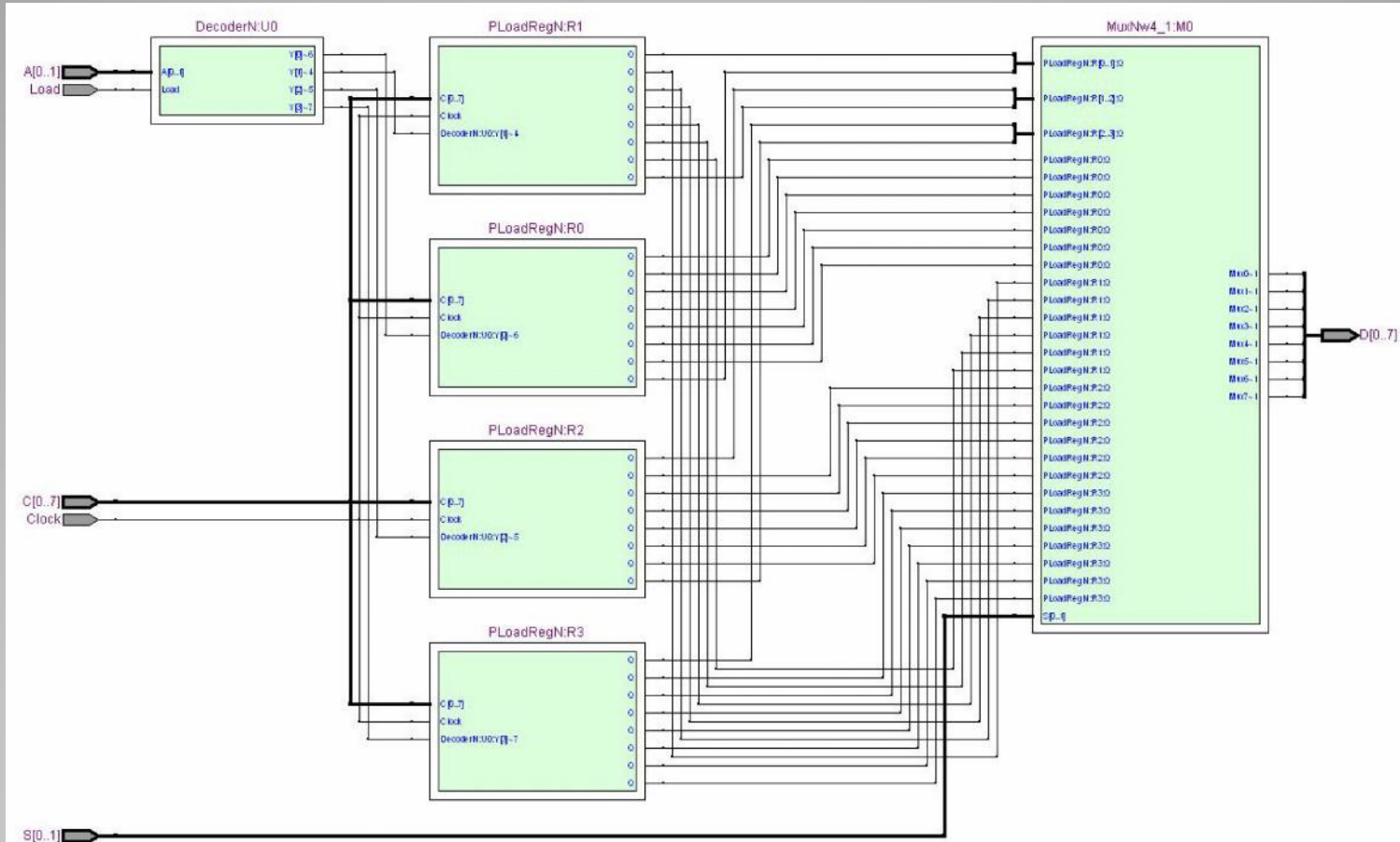

# What Quartus Built