

Introduction to Sequential Circuits

Latches
Flip-flops
Registers

- Combinational circuit

Output depends only on present inputs

Example: Half adder

- Sequential circuit

Output depends not just on present inputs, but on past sequence of inputs

Stores information, also known as having "state"

Simple example: a circuit that counts up in binary

Definitions


A flip-flop is Edge sensitive: Output only changes on rising (or falling) edge of clock.
A latch is Level sensitive: Output changes whenever clock/Enable is high (or low)

A common implementation of a flip-flop is a pair of latches (Master/Slave flop).

Latches are sometimes called “transparent latches”, because they are transparent (input directly connected to output) when the clock is high.


The clock to a latch is primarily called the “enable”.

 For more information have a look at the picture below.




From The Digital Electronics Blog

Latch vs Flip-flop

 

 Designer does not have to worry about S and R both being 1 by the addition of an inverter.




D latch symbol

Level-Sensitive D-Latch

```
module D_Latch (D, Clk, Q);  
    input D, Clk;  
    output reg Q;  
  
    always @(D, Clk)  
        if (Clk)  
            Q = D;  
  
endmodule
```

- If you enter this in Quartus, you'll get several warnings (**inferred latches**)
- We really don't want **inferred latches**.
- If you want a latch, use the Quartus primitive (shown later)

Figure 7.35. Code for a gated D latch.

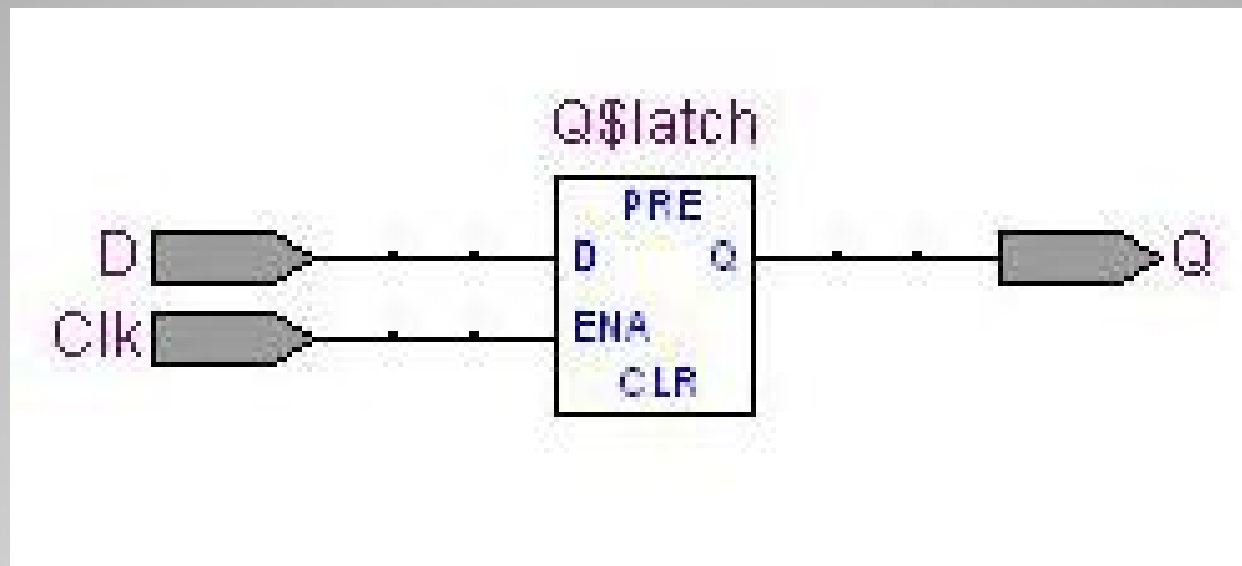

What Quartus Built
RTL View

```
module D_Latch (D, Clk, Q);  
    input D, Clk;  
    output Q;  
  
    latch D1( D, Clk, Q );  
    //LATCH <instance_name> (.d(<input_wire>),  
    //      .ena(<input_wire>), .q(<output_wire>));  
    // latch D2( .d(D), .ena(Clk), .q(Q) );  
  
endmodule
```

(Quartus built the same circuit as previously shown)

D-Latch Using Quartus Primitive

- D latch still has problem (as does SR latch)


When $C=1$, through how many latches will a signal travel?

Depends on for how long $C=1$

- Clk_A -- signal may travel through multiple latches
- Clk_B -- signal may travel through fewer latches




Hard to pick C that is just the right length

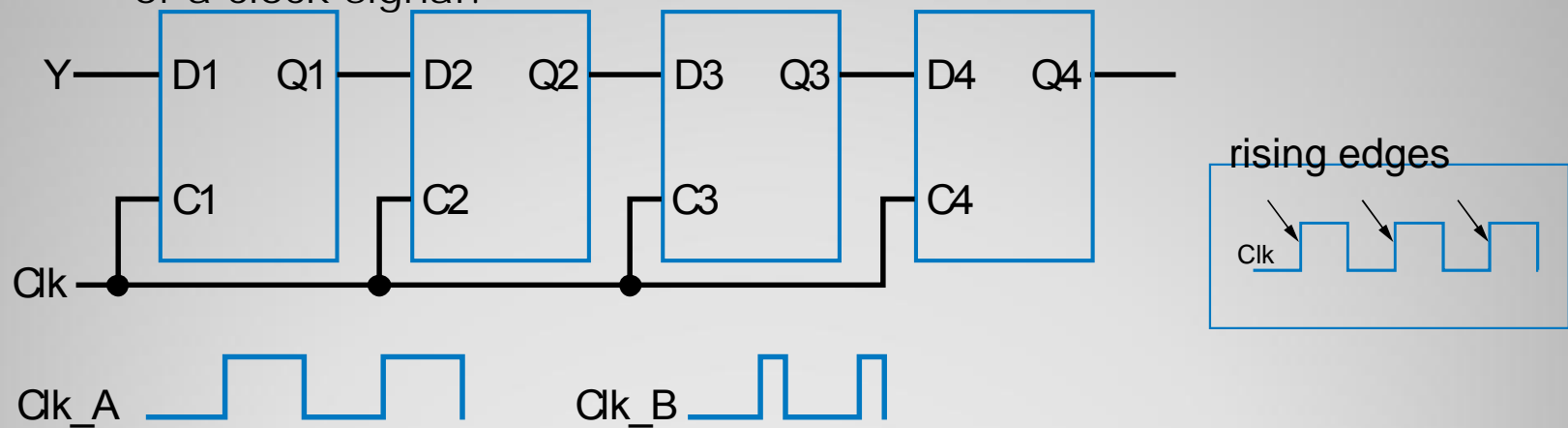- Can we design bit storage that only stores a value on the rising edge of a clock signal?




Problem with Level-Sensitive D Latch: Attempted Shift Register

Chart from F. Vahid

   


Positive Edge DFF

or

 

Negative Edge DFF

The D-Flip-Flop Solution

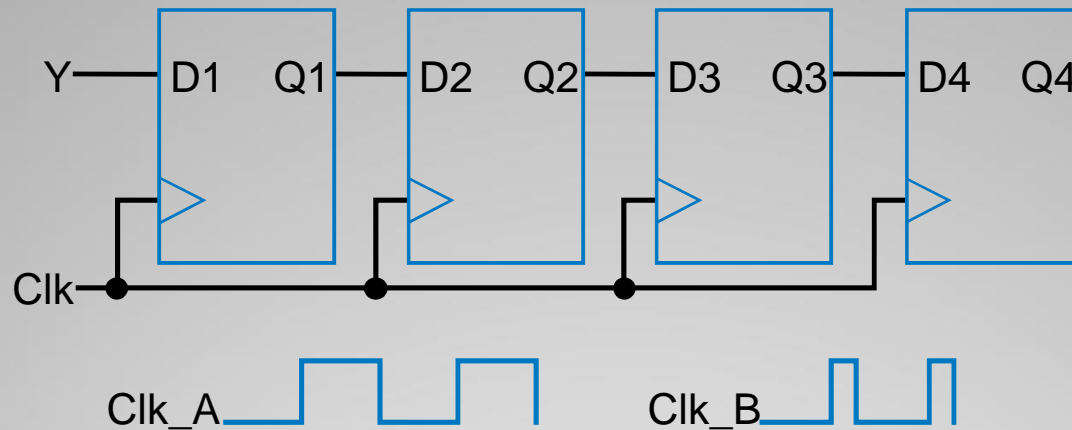


Solves the problem mentioned earlier: Data will advance exactly one FF per (positive) clock edge, regardless of the clock period or duty cycle.

D Flip-Flops Wired Together: Correct Shift Register

```
module DFlipFlop( D, Clock, Q );  
  input D, Clock;  
  output reg Q;  
  
  always @( posedge Clock )  
    Q <= D;  // non-blocking  
  
endmodule
```

Figure 7.36. Code for D flip-flop

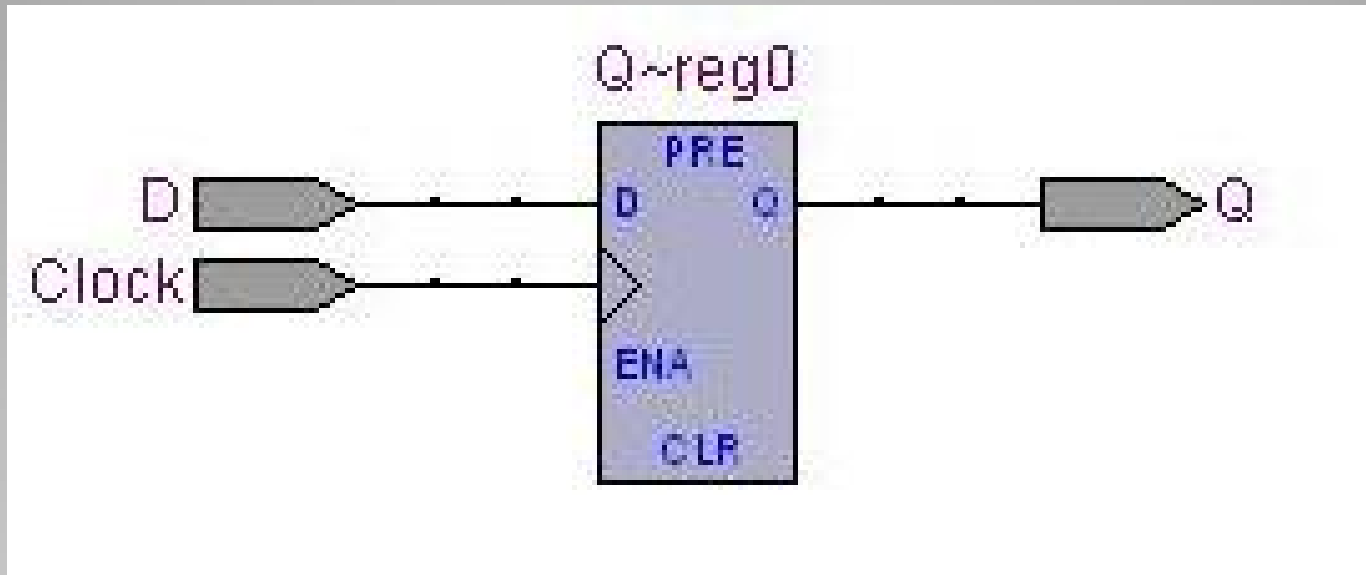

Note the unused ports (inputs):

- ENA = Enable
- CLR = Clear
- PRE = Preset (opposite of Clear)

What Quartus Built
(RTL View)

Deprecated Hardware:

Latches:

1. Use flops, not latches
2. Latch-based designs are susceptible to timing problems
3. The transparent phase of a latch can let a signal “leak” through a latch — causing the signal to affect the output one clock cycle too early
4. It's possible for a latch-based circuit to simulate correctly, but not work in real hardware, because the timing delays on the real hardware don't match those predicted in synthesis

Flip-flops:

1. Limit yourself to D-type flip-flops
 2. Some FPGA and ASIC cell libraries include only D-type flip flops. Others, such as Altera's APEX FPGAs, can be configured as D, T, JK, or SR flip-flops.
- For every signal in your design, know whether it should be a flip-flop or combinational. Examine the log file e.g. dc shell.log to see if the flip-flops in your circuit match your expectations, and to check that you don't have any latches in your design.
 - Do not assign a signal to itself (e.g. `a <= a;` is bad). If the signal is a flop, use an enable to cause the signal to hold its value. If the signal is combinational, then assigning a signal to itself will cause combinational loops, which are very bad.

Some Advice



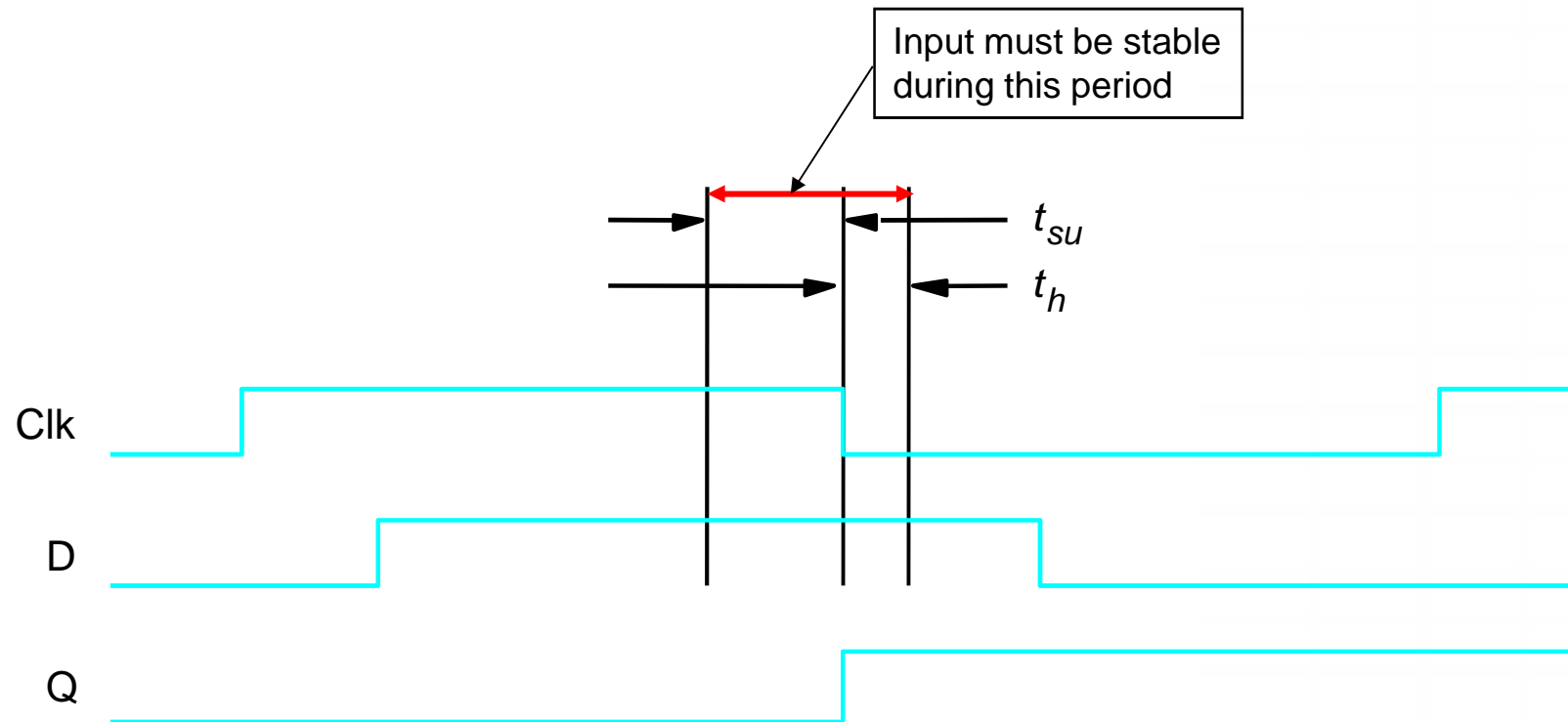


Figure 7.9. Setup and hold times.

 


Setup and negative hold times.

 


```
module example7_3 (D, Clock, Q1, Q2);  
    input D, Clock;  
    output reg Q1, Q2;  
    always @(posedge Clock)  
    begin  
        Q1 = D;    // blocking  
        Q2 = Q1;  
    end  
endmodule
```

Two cascaded flip-flops

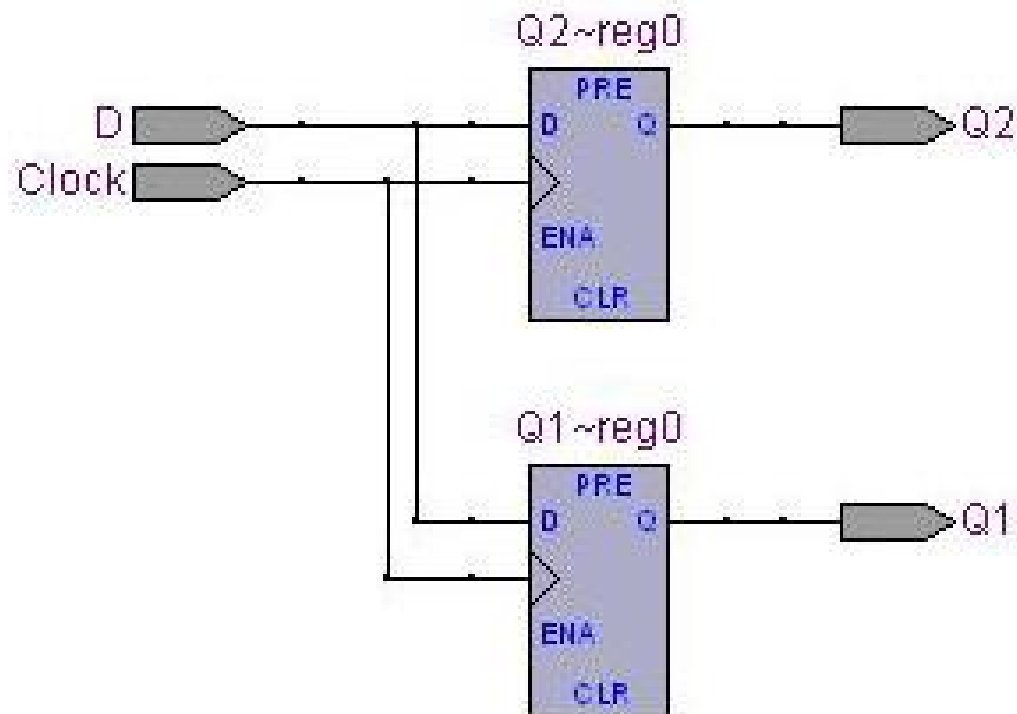


What Quartus Built

 

```
module example7_3 (D, Clock, Q1, Q2);  
  input D, Clock;  
  output reg Q1, Q2;  
  always @(posedge Clock)  
  begin  
    Q1 <= D; // non-blocking  
    Q2 <= Q1;  
  end  
endmodule
```

Figure 7.37. Correct code for two cascaded flip-flops

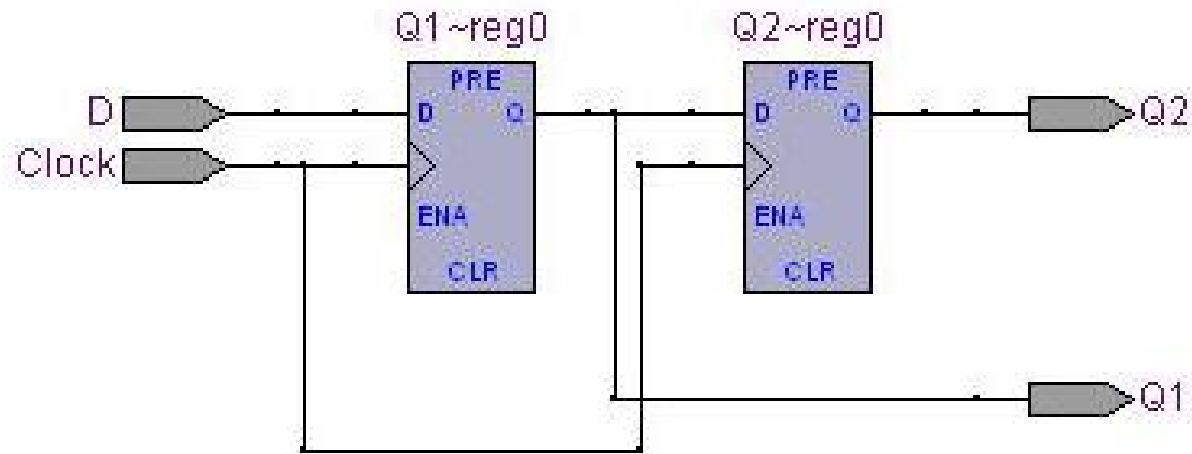

What Quartus Built

- Use blocking assignments ($=$) to model combinational logic.
- Use non-blocking assignments ($<=$) to model sequential logic.
- This helps avoid race conditions that can develop.



Blocking/Non-blocking Uses

[Middle English *registre*, from Old French, from Medieval Latin *registrum*, alteration of Late Latin *regesta*, from Latin neuter pl. past participle of *regerere*, to record : *re-*, *re-* + *gerere*, to carry.]


Origin of 'register'

- A **Register** is a collection of bit storage flip-flops as shown below.
- Each Q is brought out to a pin; they are not cascaded together.
- Assembly programmers are familiar with the term **Register**.
- In Verilog:
  
```
...
reg [3:0] A;
always @( posedge Clk ) begin
    A <= X;  // non-blocking
end
...
```



Basic Register

 

```

module TFFx( T, Clk, ClrN, Q, QN );
  input T, Clk, ClrN;
  output reg Q;
  output QN = ~Q;
  always @( posedge Clk ) begin
    if ( T ) Q <= ~Q;
    else Q <= Q;
  end // need to implement Clear
endmodule

```

Note: TFF and tff are Quartus primitive names, so we can't use these for our module names.

T-Flip Flop (Toggle Flip Flop)

```
module TFFx( T, Clk, ClrN, Q, QN );
  input T, Clk, ClrN;
  output reg Q;
  output QN = ~Q;
  always @( posedge Clk ) begin
    if ( ~ClrN )
      Q <= 1'b0;
    else
      if ( T )
        Q <= ~Q;
      else
        Q <= Q;
    end
  end
endmodule
```

TFF with Clear


 


Figure 1. A 4-bit counter.

Counter out of TFFs

 

ModelSim Output

```
reg Clk;  
always begin  
    Clk = 0;  
    #10;  
    Clk = 1;  
    #10;  
end
```

This clock (Clk) would have a period of 20 time units

How to Generate a Clock Signal in ModelSim