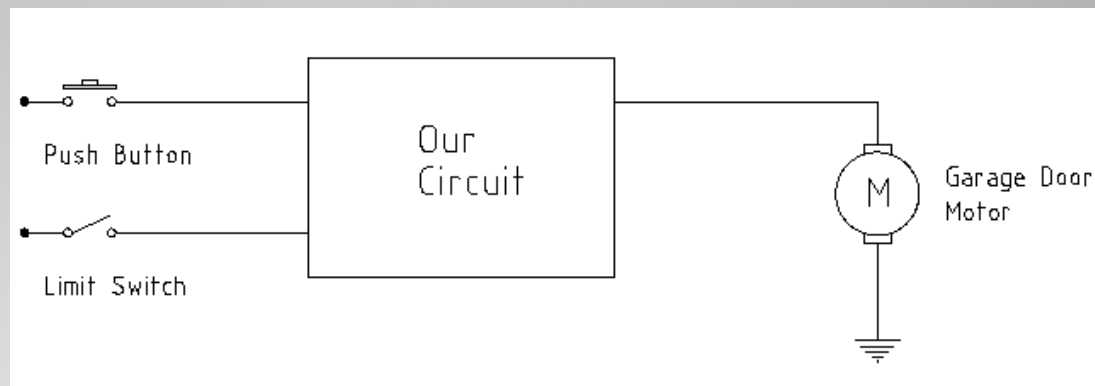


State Machines Introduced

Lecture 8


- “Brains of the outfit”
- Use registers to save current state.
- Used to control datapath components
- In Verilog we build state machines pretty much like we would in software.

Finite State Machines




We want a circuit that fully opens the garage door when the push-button is momentarily pressed. Limit switch turns off the motor.

Garage Door Example

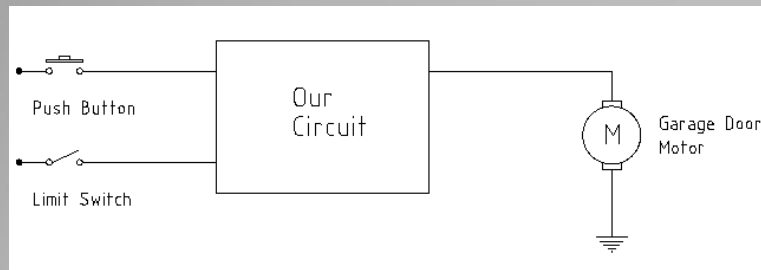


Truth Table for Motor Circuit FF

Push-Button	Limit Switch	Current Q	D (next Q)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

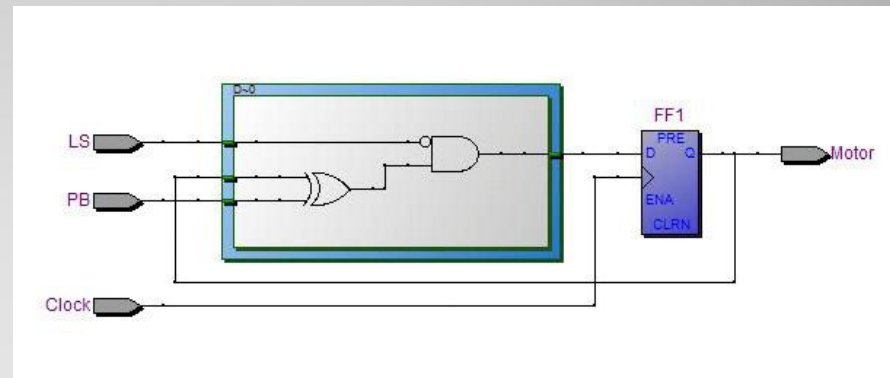


 Garage Door Circuit Using
D Flip-Flop (TCES 220 Method)



Motor State = M
Pushbutton State = PB
Limit Switch state = LS

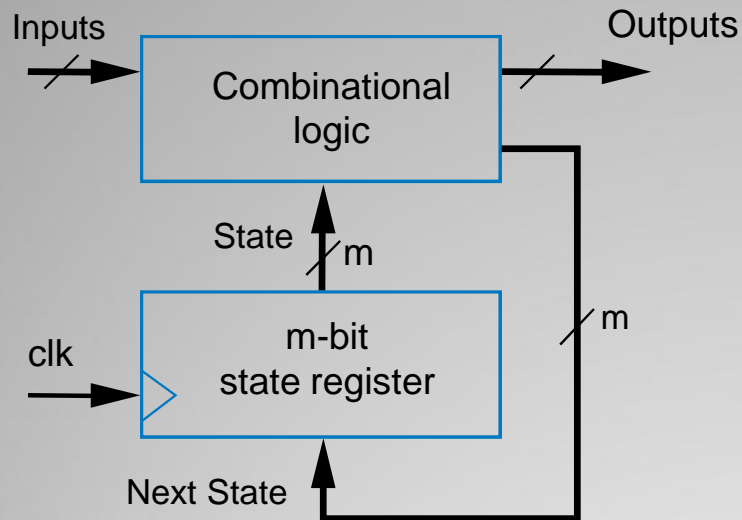Garage Door Opener States and Transitions



General FSM Architecture

You are used to forming the truth table (TT) for the combinational part:



- Inputs to TT would be the FSM inputs plus the current state
- Outputs to the TT would be the FSM outputs plus the next state

Verilog Code Design (Architecture)

- Name states with localparams
- Have State and NextState reg variables of the correct size
- Have a combinational loop and a sequential loop
- Combinational Loop
 - Set all variables to default values
 - Have a case for each state
 - Have a default case
- Sequential Loop
 - State <= NextState
 - Take care of Reset here


SM Rules of Thumb

 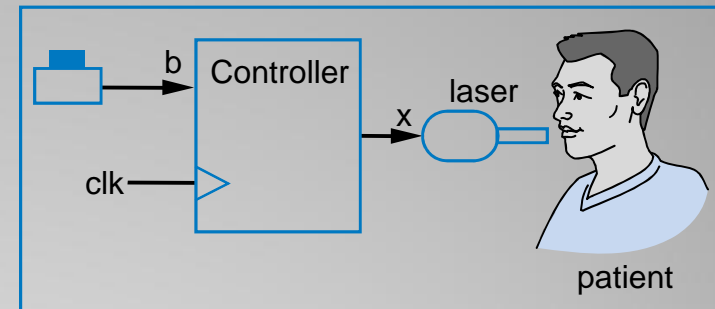- Consider a laser surgery system
- Laser should be ON exactly 30 ns
- Assume a clock with a 10 ns period
- Example system where software in a μ Processor is not such a good idea.



Transitions only on clock edges

Example FSM

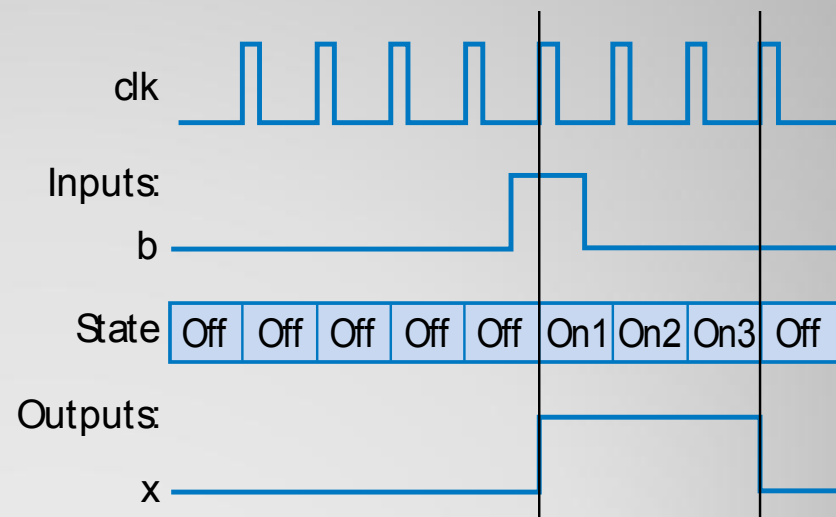

From F. Vahid's Digital Design, 2007


```
module LaserSM( B, X, Clk, Rst );  
    input B;  
    input Clk, Rst;  
    output reg X;  
  
    // State Name assignments  
    localparam S_Off = 0,  
               S_On1 = 1,  
               S_On2 = 2,  
               S_On3 = 3;  
  
    reg [1:0] State, StateNext;
```

Verilog Laser Surgery FSM, Front
end

```
// CombLogic (use blocking assignments)
always @ ( State, B ) begin
    case (State)

        S_Off: begin
            X = 0; // laser OFF
            if ( B == 0 ) begin
                StateNext = S_Off; // button not pushed
            end
            else begin
                StateNext = S_On1; // button pushed
            end
        end

        S_On1: begin
            X = 1; // laser ON
            StateNext = S_On2; // always go to next state
        end
    end
```

Combinational Logic Part

```
S_On2: begin
    X = 1; // laser ON
    StateNext = S_On3; // always transition to next state
end



S_On3: begin
    X = 1; // laser still ON
    StateNext = S_Off; // always transition to off state
end

default: begin
    X = 0;
    StateNext = S_Off;
end
endcase
end // always
```

Combinational Logic, cont.


```
// StateReg (use non-blocking assignments)
always @( posedge Clk ) begin
    if ( Rst == 1 ) begin
        State <= S_Off;      // reset overrides everything else
    end
    else begin
        State <= StateNext; // otherwise go to the state we set
    end
end // always
endmodule
```

State Register

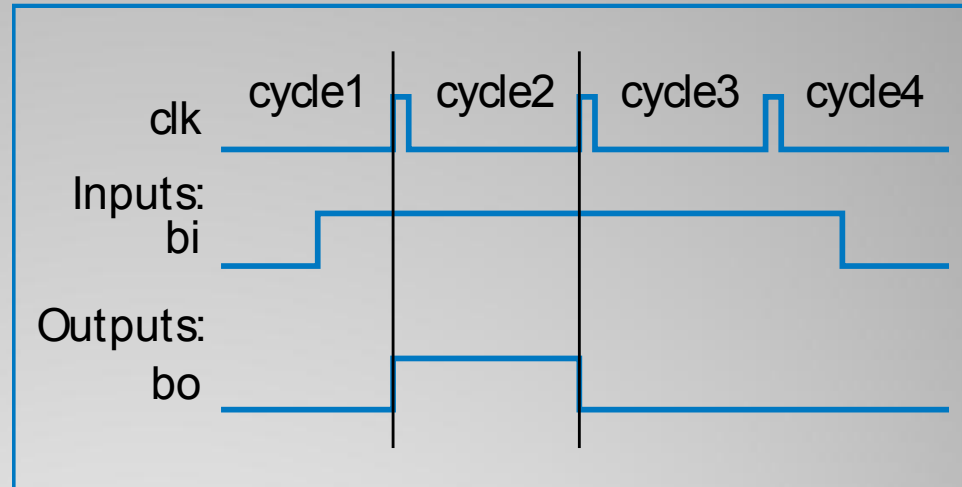 

Button Press Synchronizer

From F. Vahid's *Digital Design*, 2007

 

Button Press State Transition
Diagram

```
module ButtonSync( Bi, Bo, Clk );  
    input Bi;      // input button press  
    input Clk;     // system clock  
    output reg Bo; // our output  
  
    // State assignments  
    localparam S_A = 2'h0,  
                S_B = 2'h1,  
                S_C = 2'h2;  
  
    reg [1:0] State, StateNext;
```

Verilog for Button Synchronizer

```

// CombLogic
always @ ( State, Bi ) begin
    case (State)

        S_A: begin
            Bo = 0; // turn output OFF
            if ( Bi == 1'b1 )
                StateNext = S_B; // button push detected
            else
                StateNext = S_A;
        end

        S_B: begin
            Bo <= 1; // turn output ON
            if ( Bi == 1'b1 )
                StateNext <= S_C;
            else
                StateNext = S_A;
        end
    end

```

Combinational Part


```
S_C: begin
    Bo = 0; // turn output OFF
    if ( Bi == 1'b1 )
        StateNext = S_C; // stay in this state
    else
        StateNext = S_A; // otherwise, back to A
    end


    default: begin
        Bo = 0;
        StateNext = S_A;
    end
endcase
end // always
```

Combinational Part, cont.

```
// StateReg
always @( posedge Clk ) begin
    State <= StateNext;    // new state
end // always

endmodule
```

State Register Part

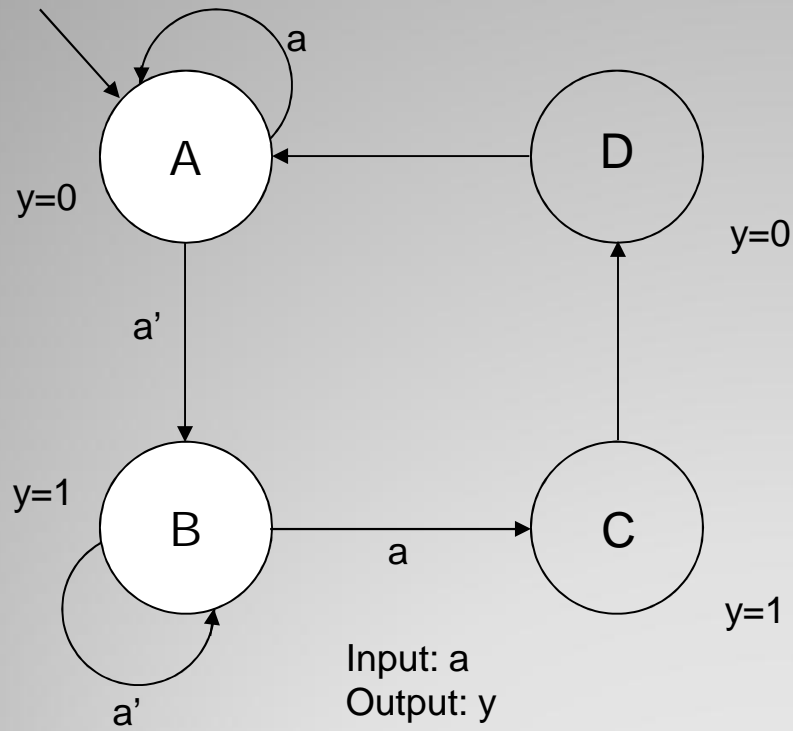

Design a Verilog module that implements the state machine shown in the diagram.

Compile your design using Quartus.

Inspect the state machine that Quartus produces and verify that it's what you expected.

Test your design using ModelSim

Can You Build This State Machine?